

Date:



EXPERIMENT NO. 4


AIM: Implement arithmetic and logic unit circuits in Logisim.



OBJECTIVES:



- i. Implement 1-bit, 2-bit, 4-bit and 8-bit arithmetic unit circuits
- ii. Implement 1-bit, 2-bit, 4-bit and 8-bit logical unit circuits for four logical functions
- iii. Implement 1-bit and 2-bit logical unit circuits for sixteen logical functions
- iv. Implement 2-bit, 4-bit and 8-bit bidirectional shifter
- v. Implement 1-bit, 2-bit, 4-bit and 8-bit ALU


CIRCUITS:

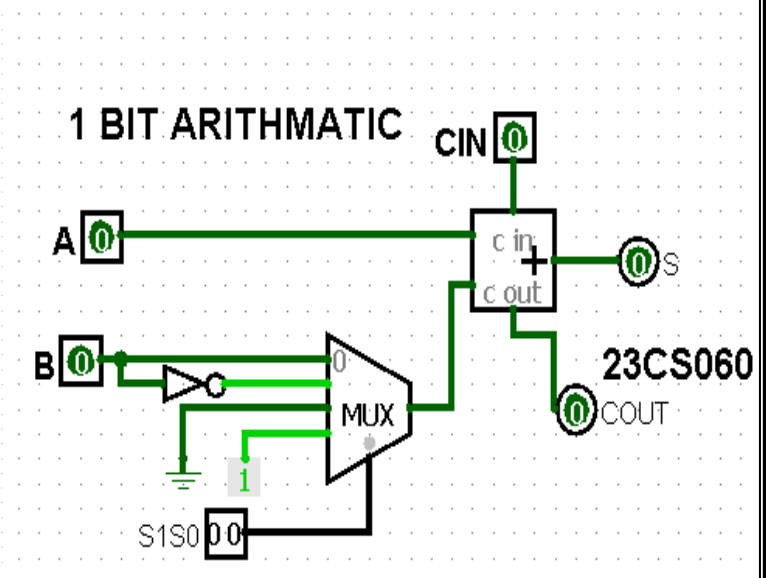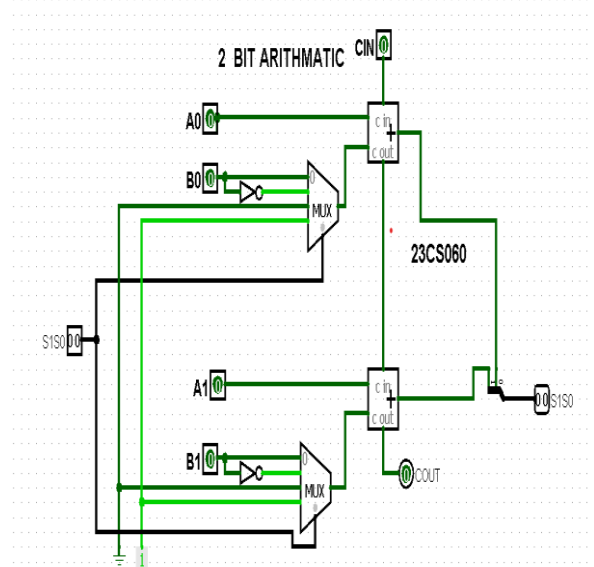



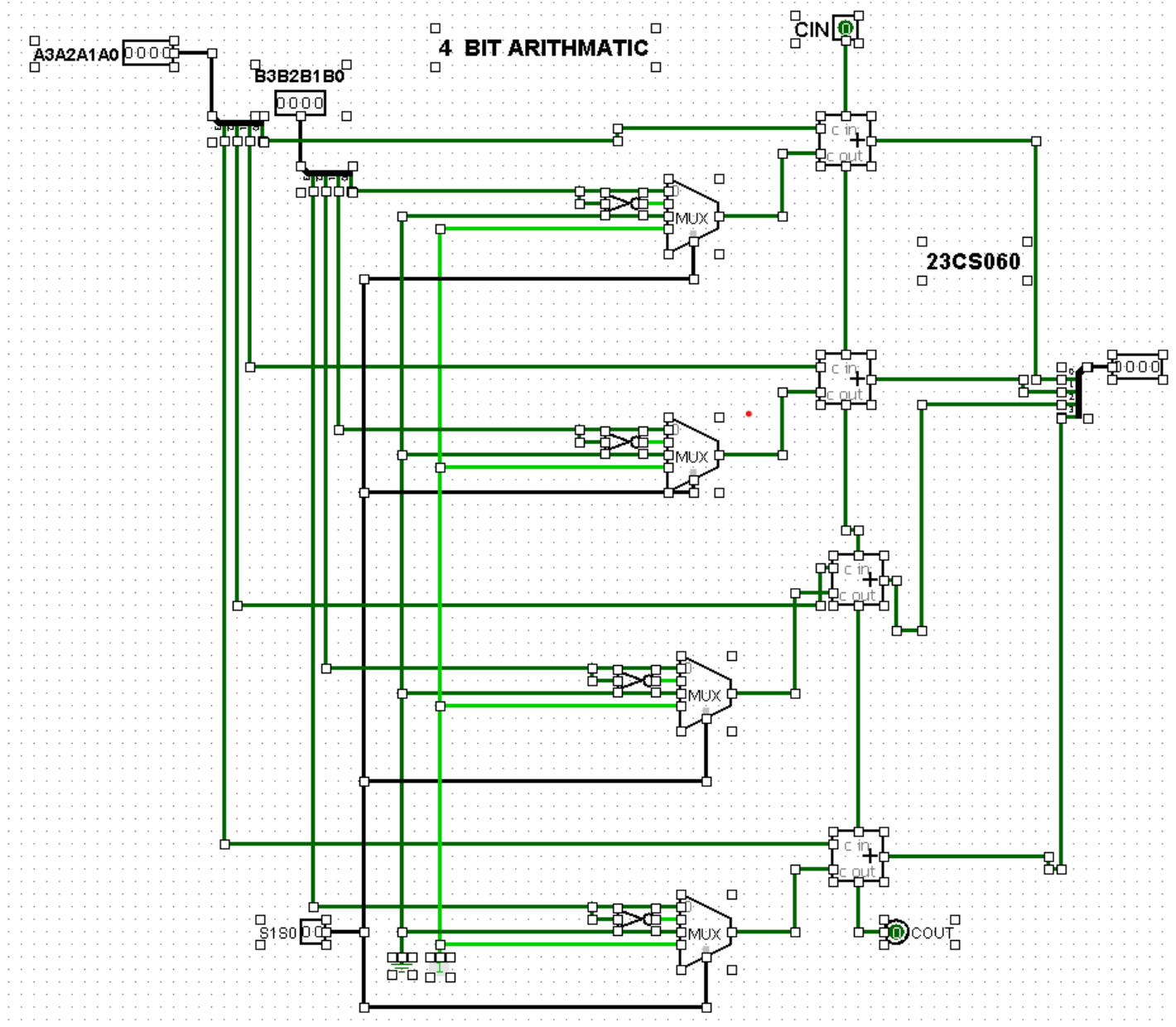


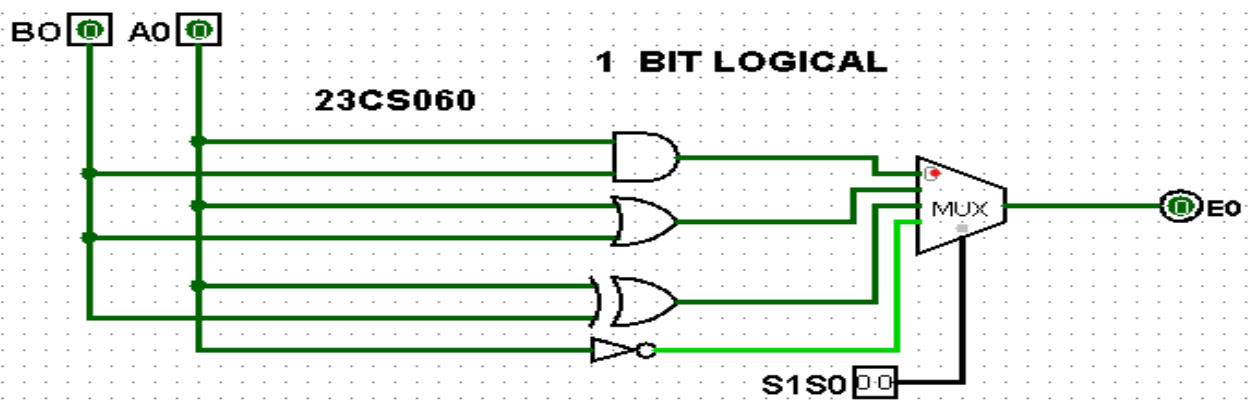
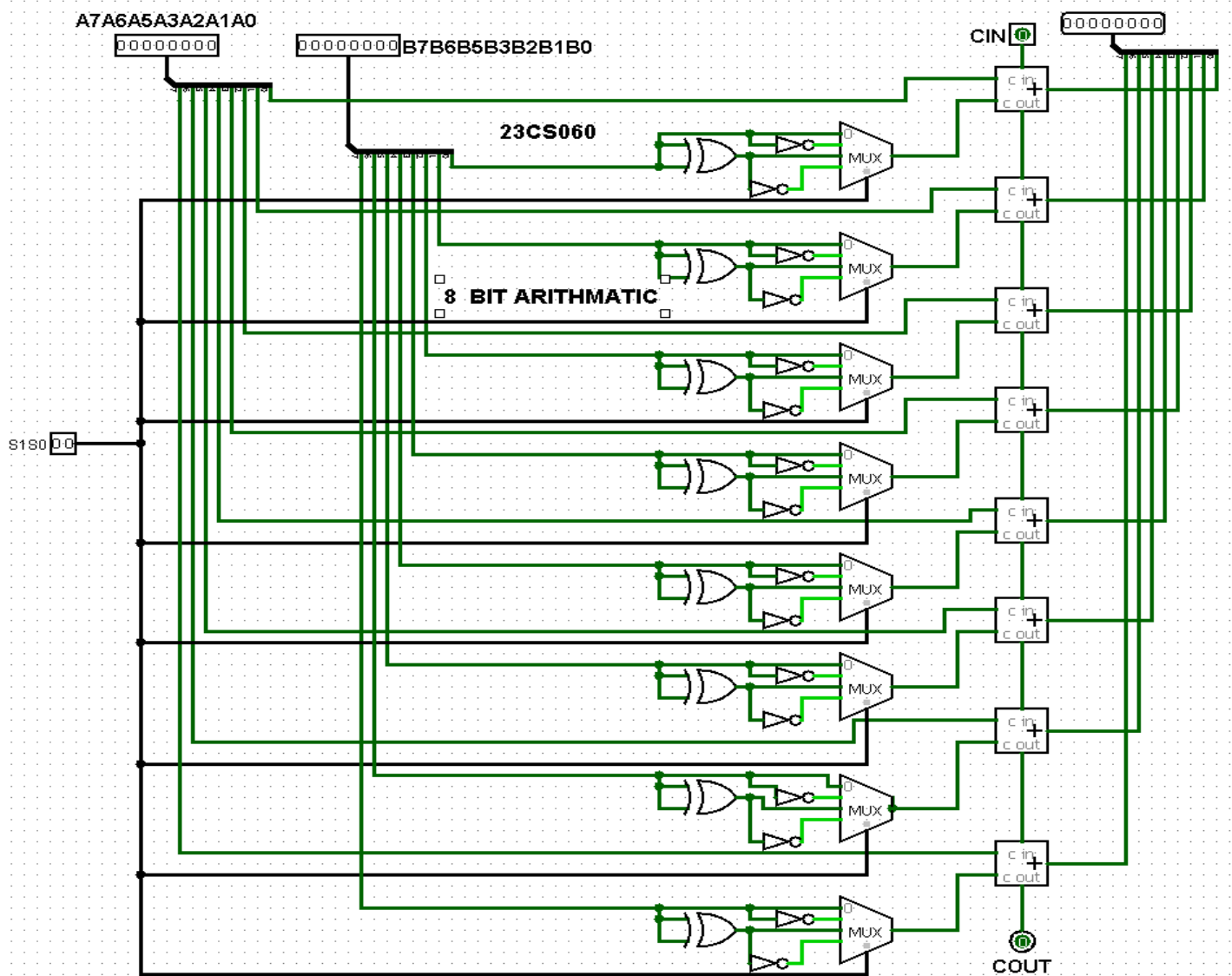


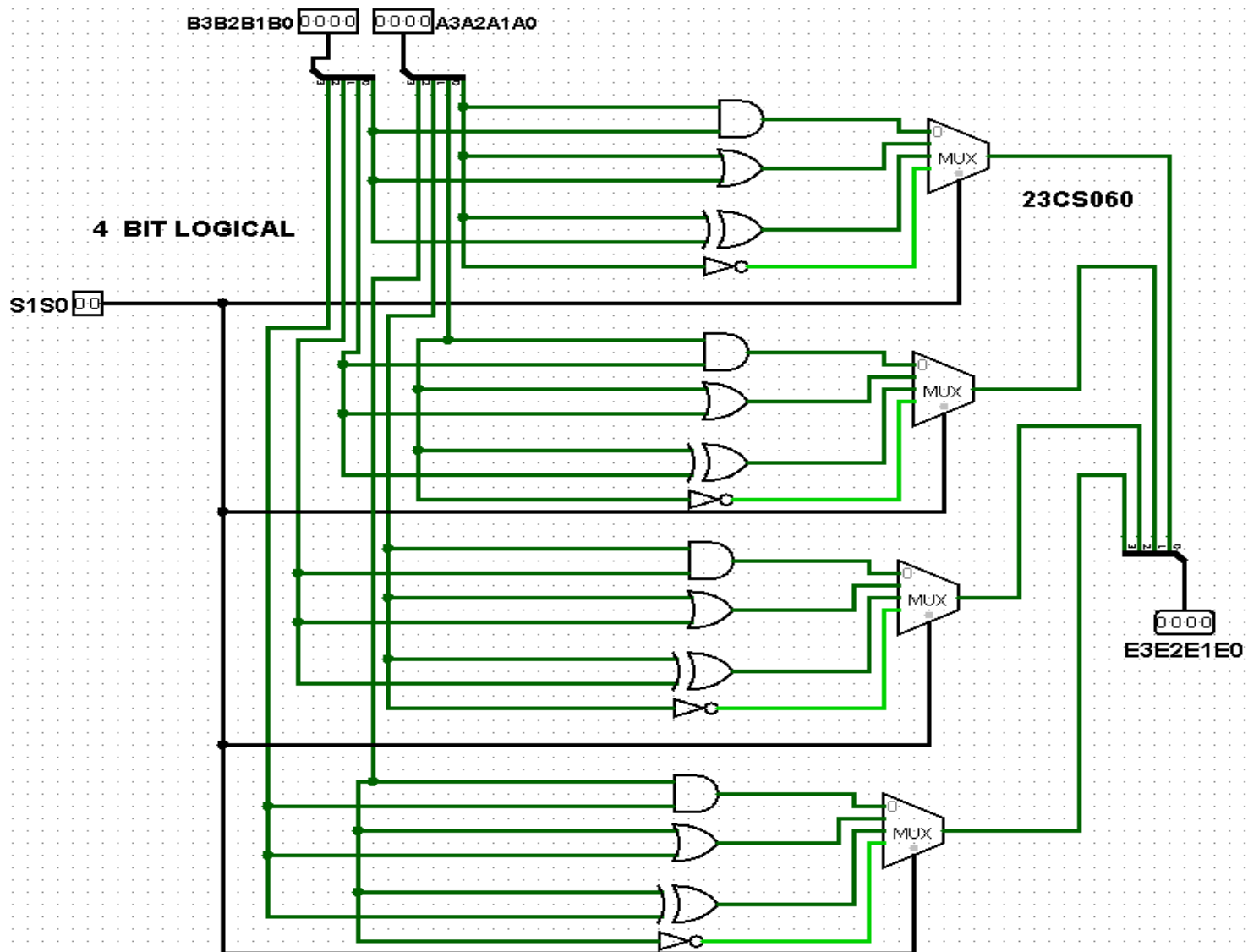
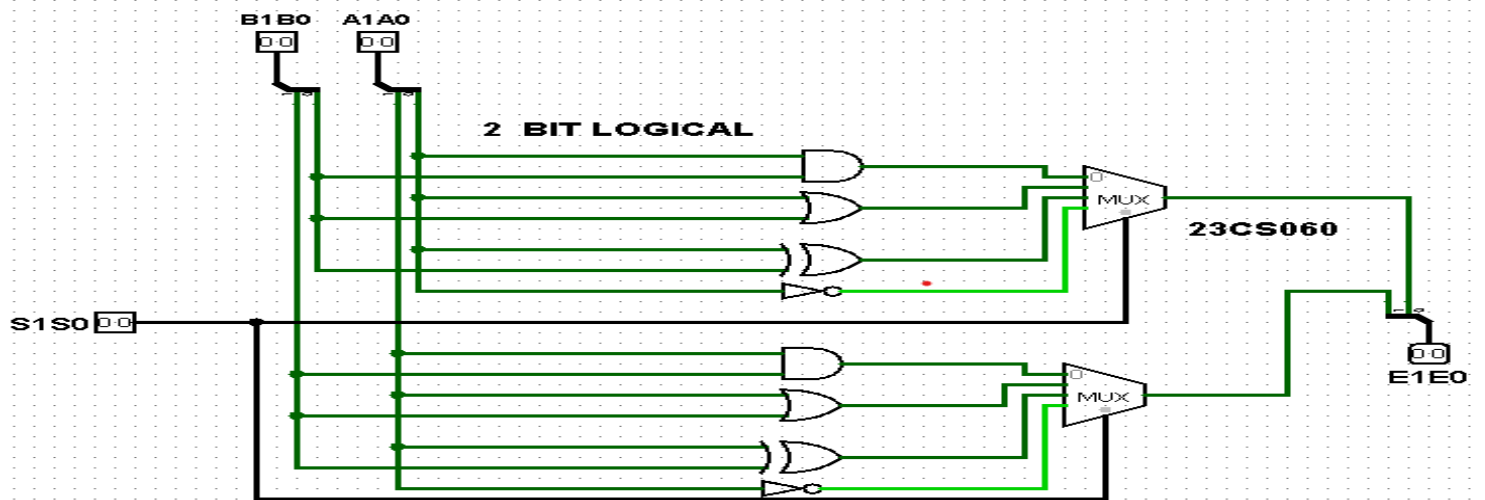


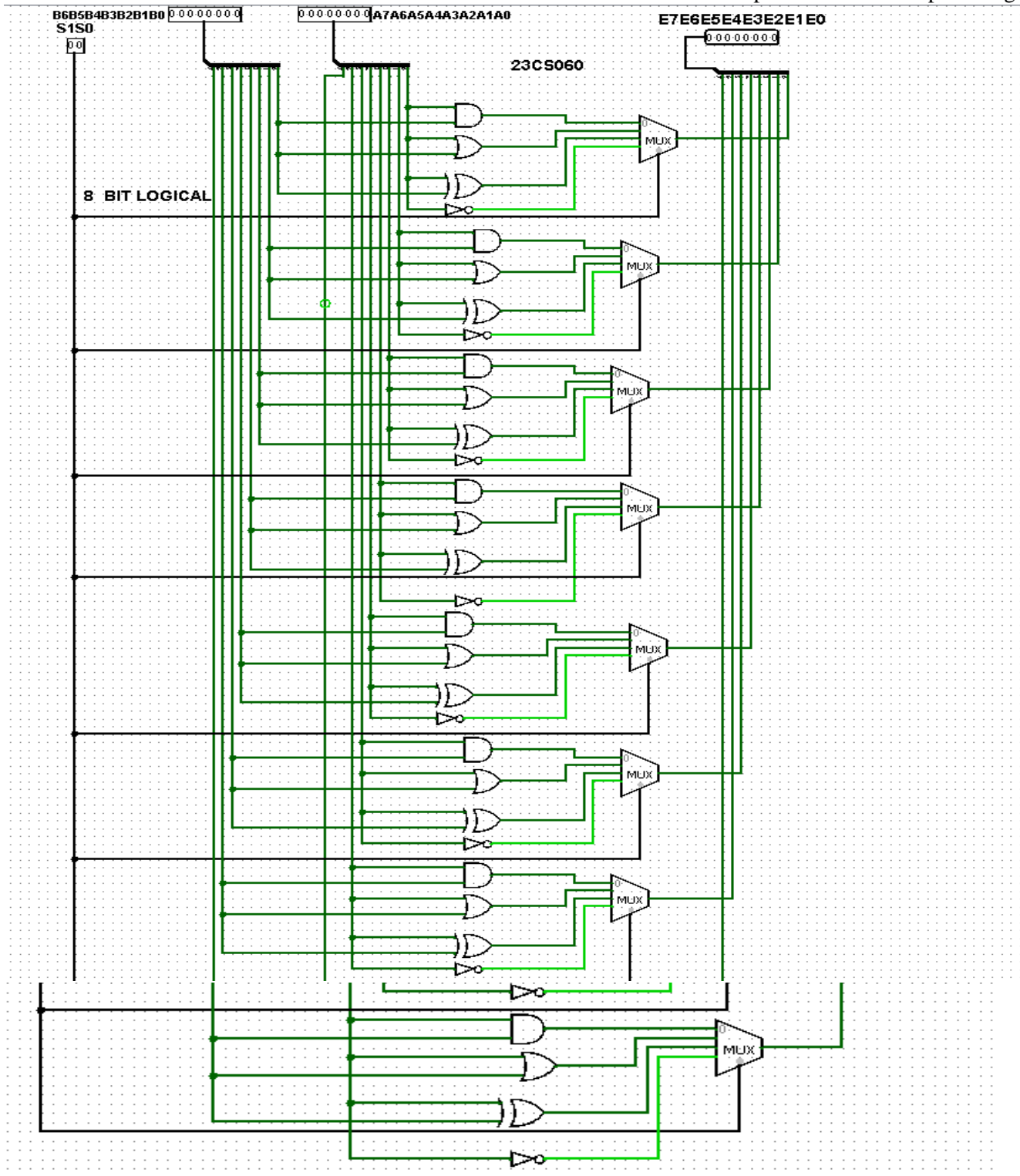


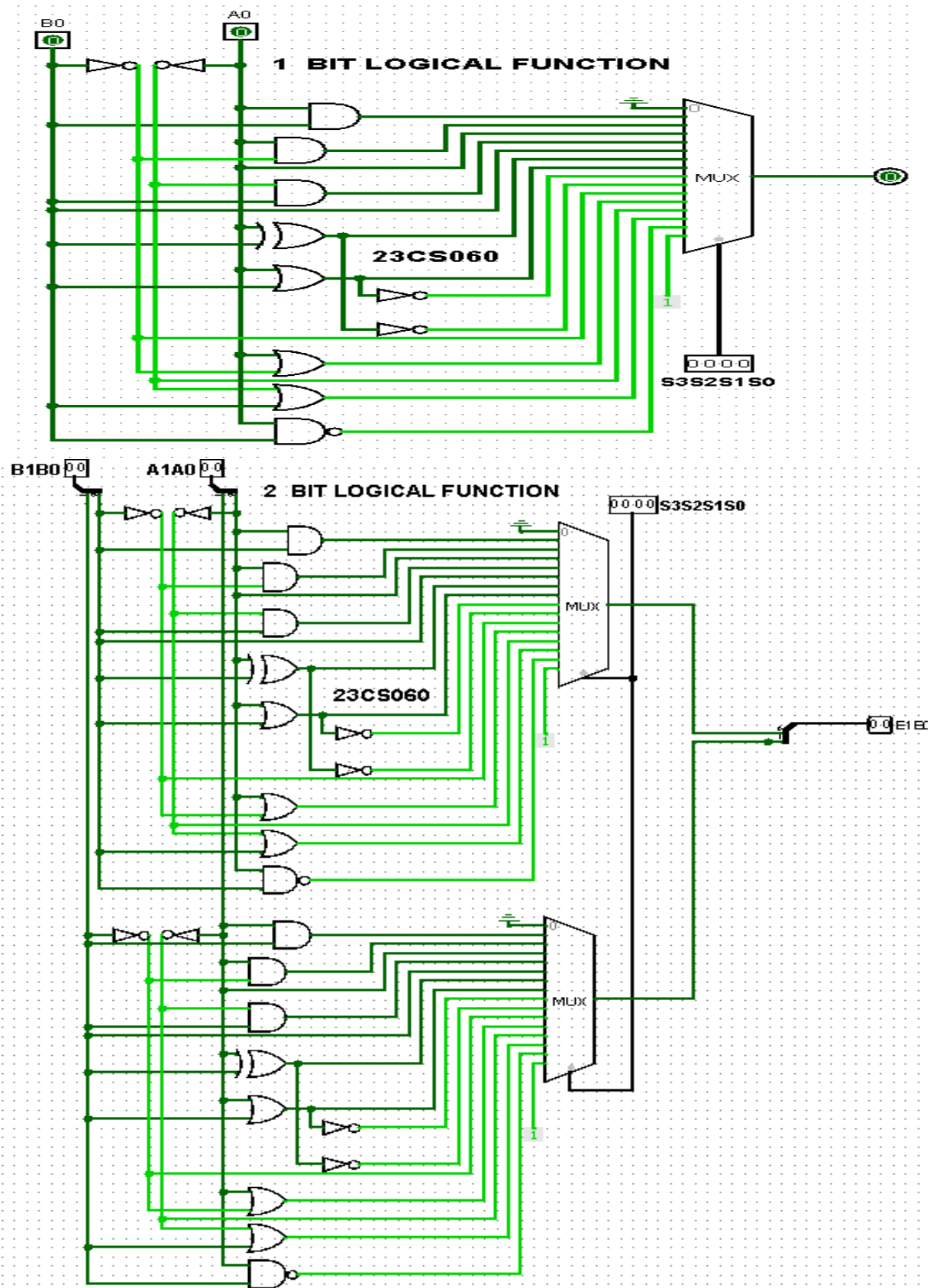

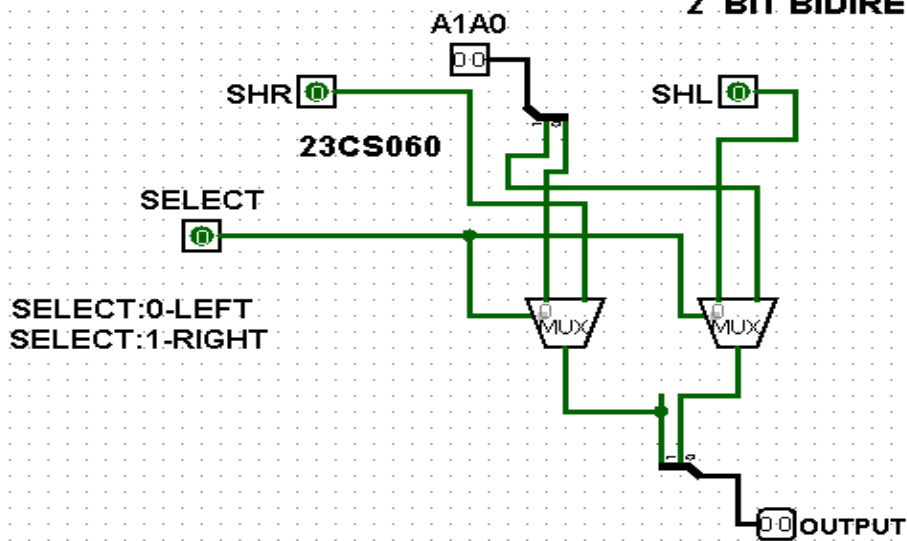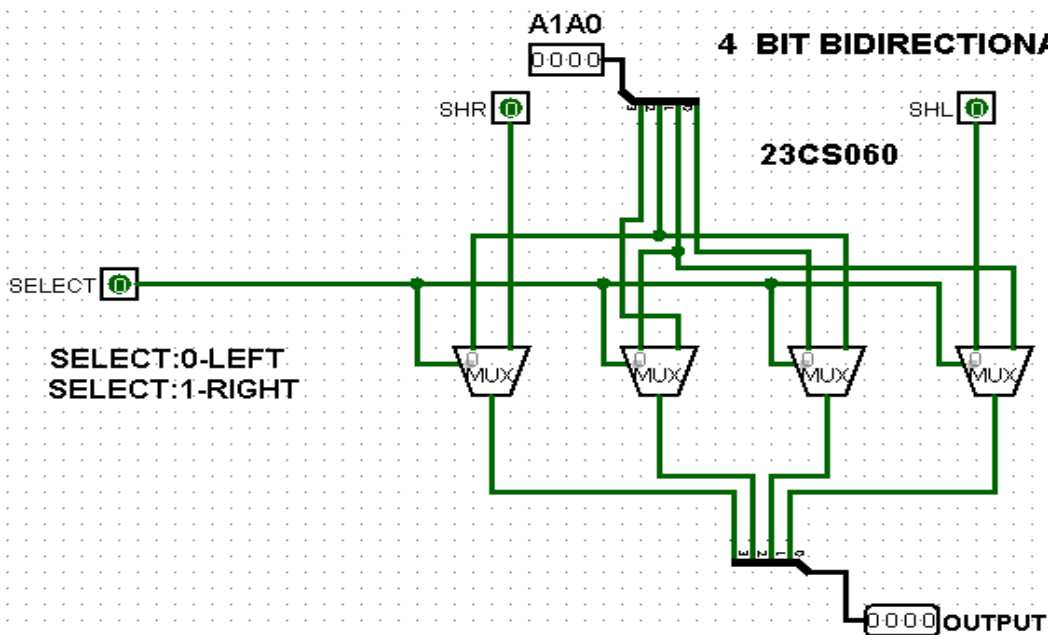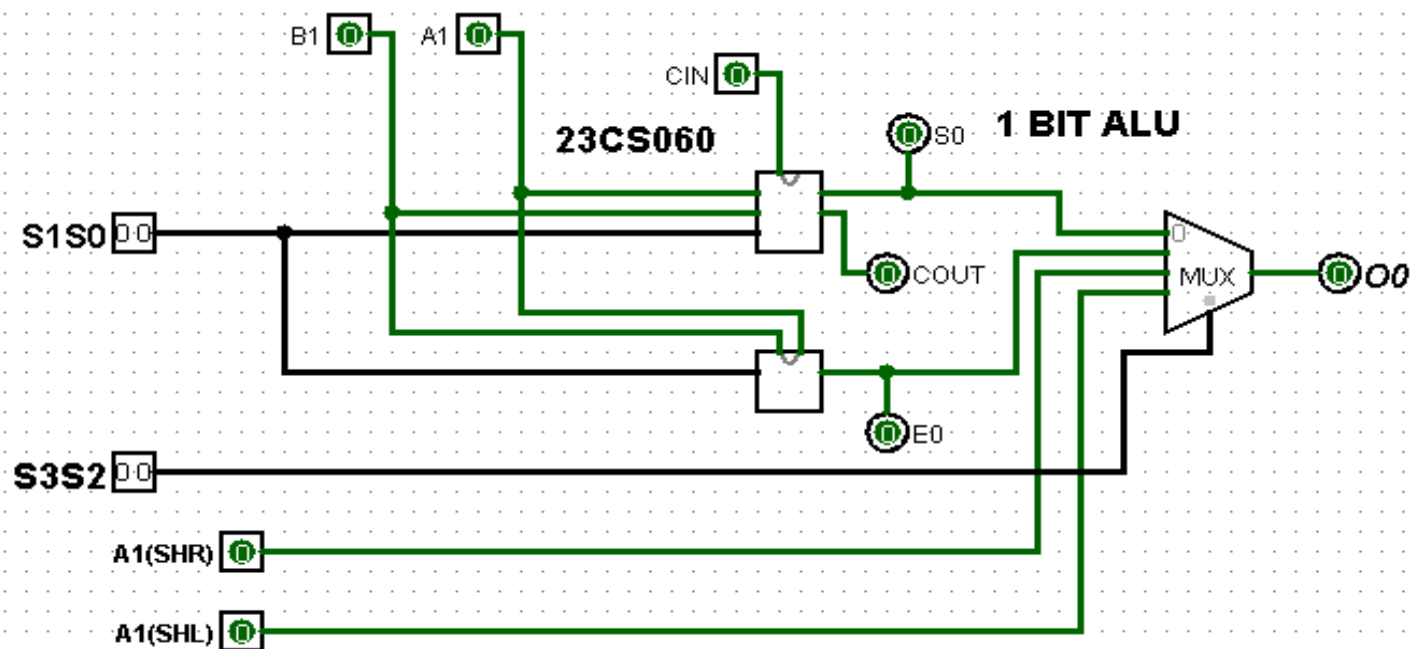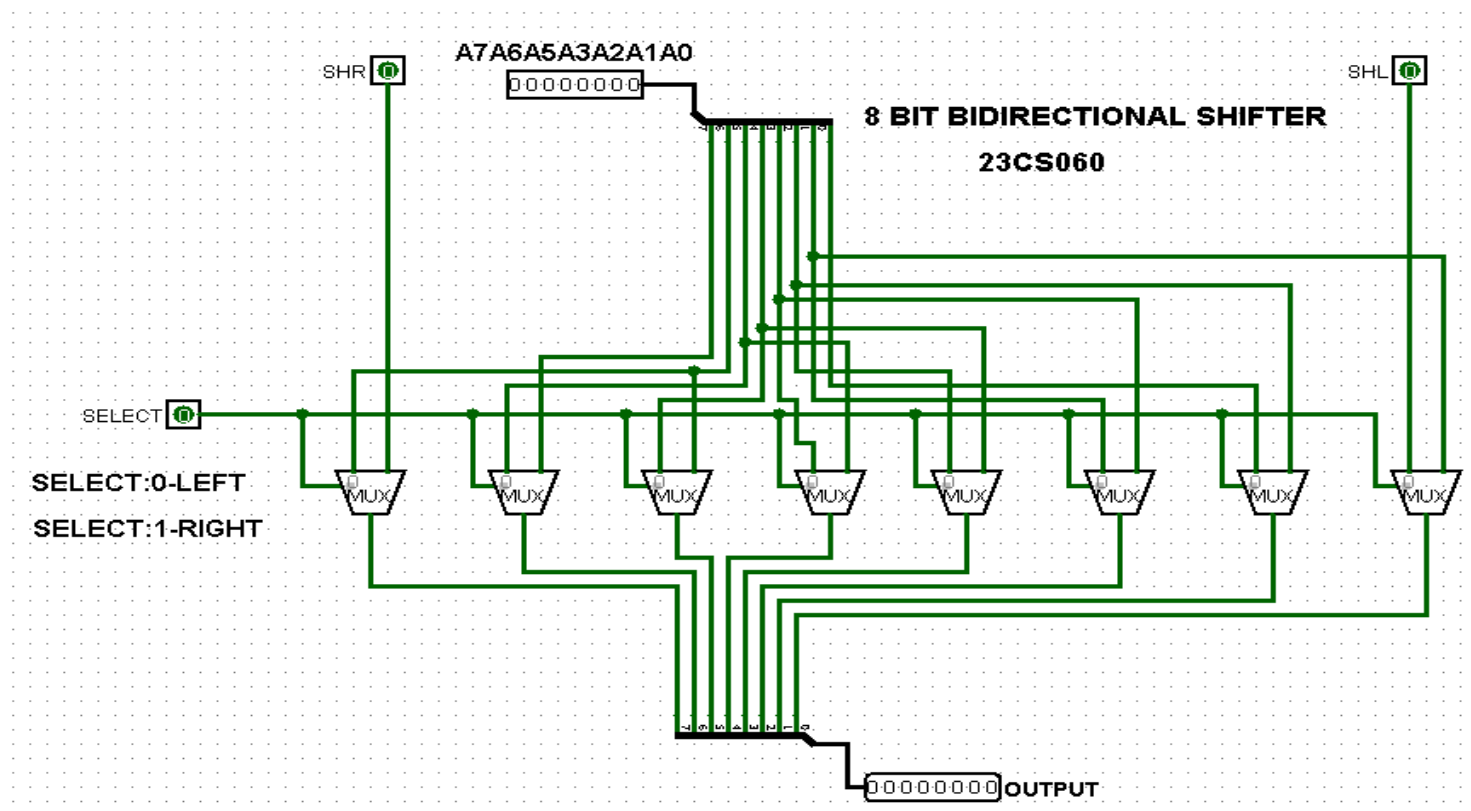
2 BIT BIDIRECTIONAL SHIFTER**4 BIT BIDIRECTIONAL SHIFTER**








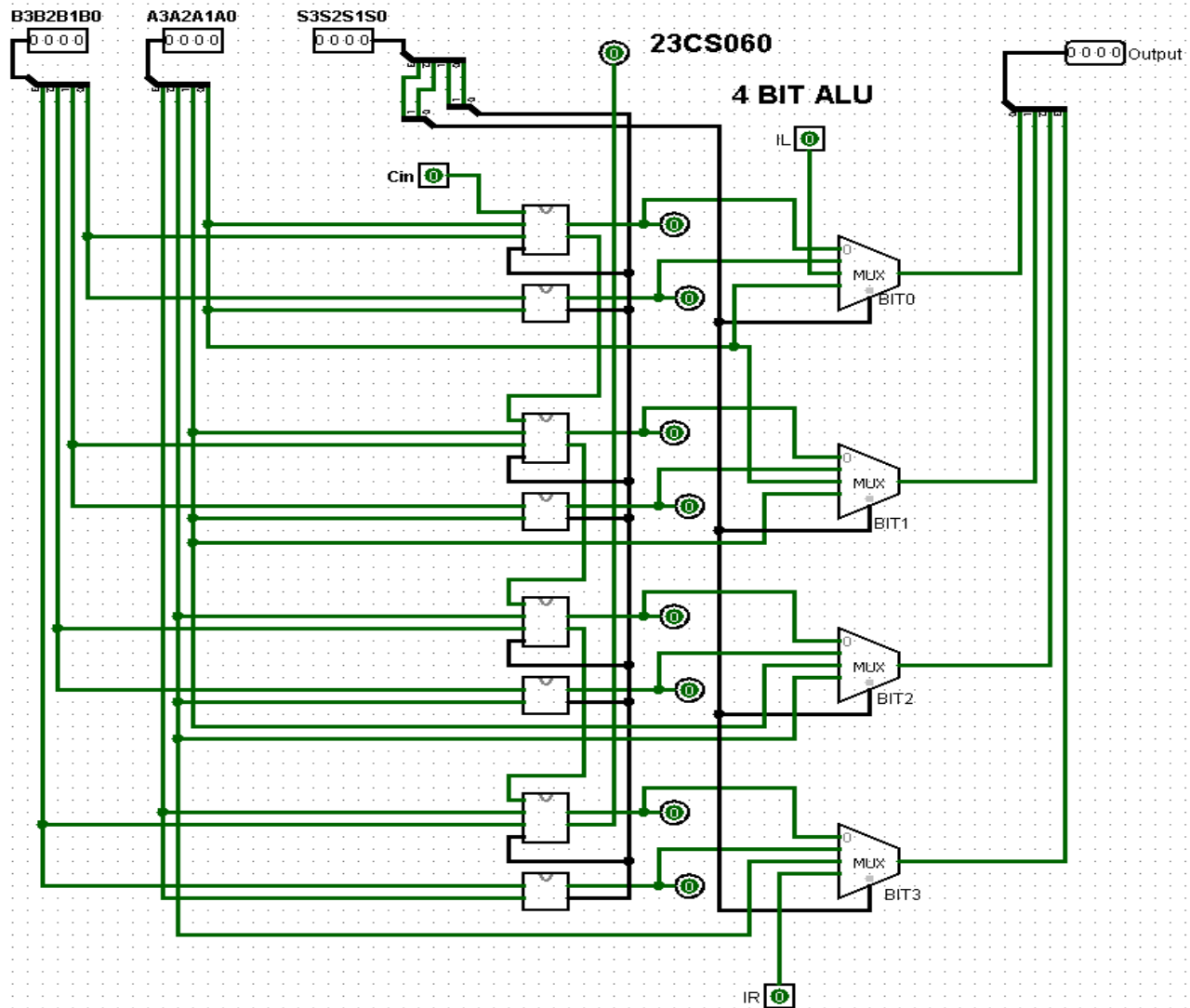
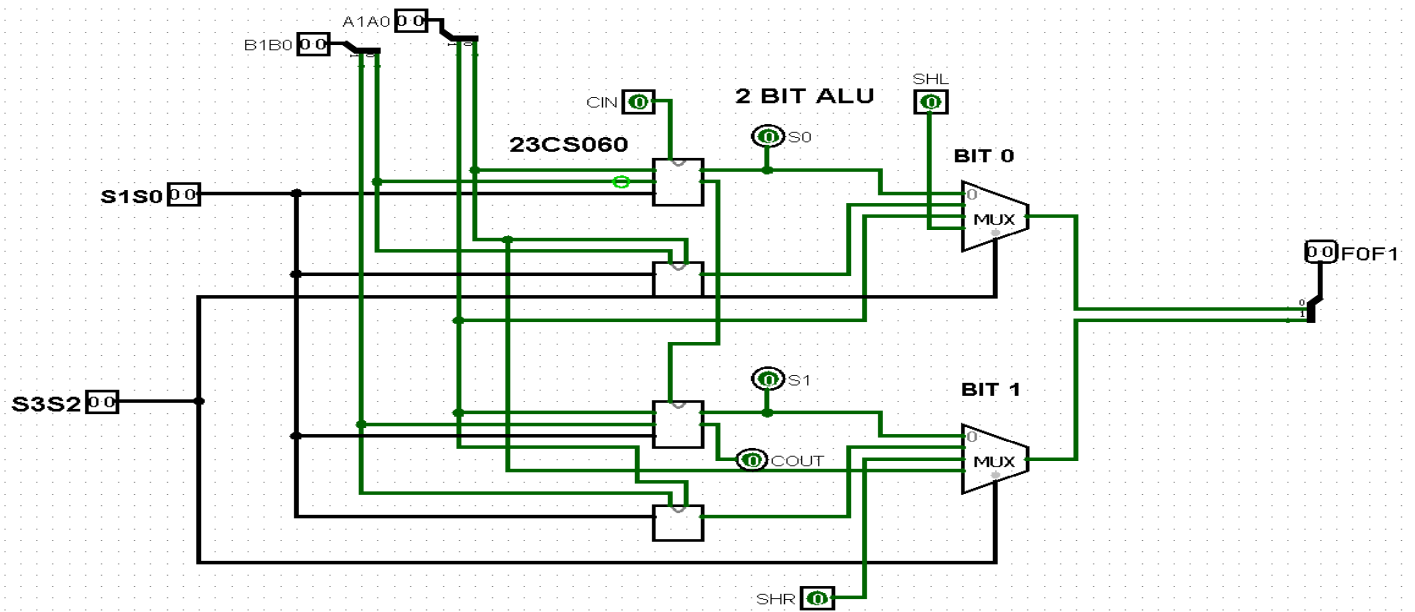





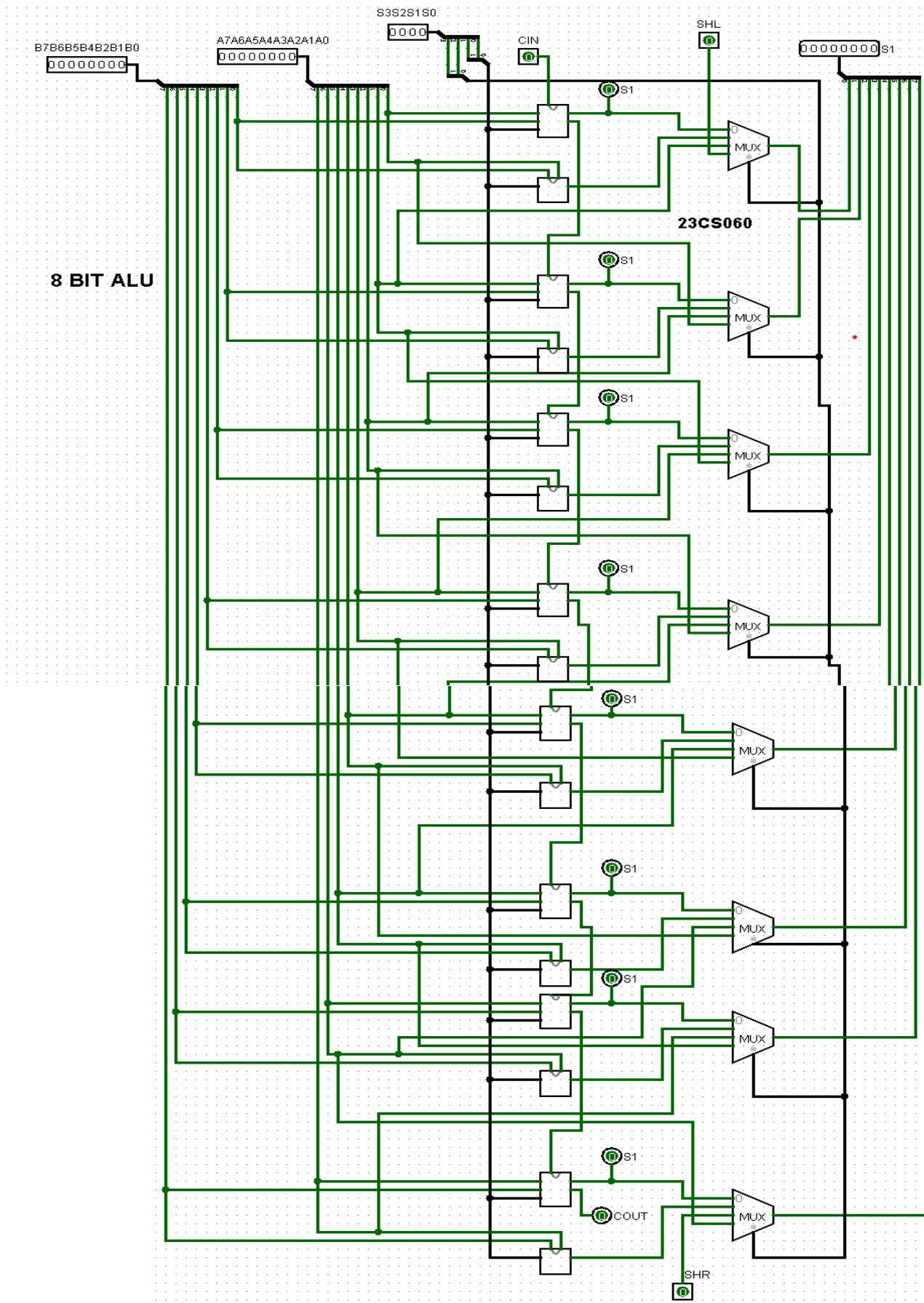







OUTPUT:

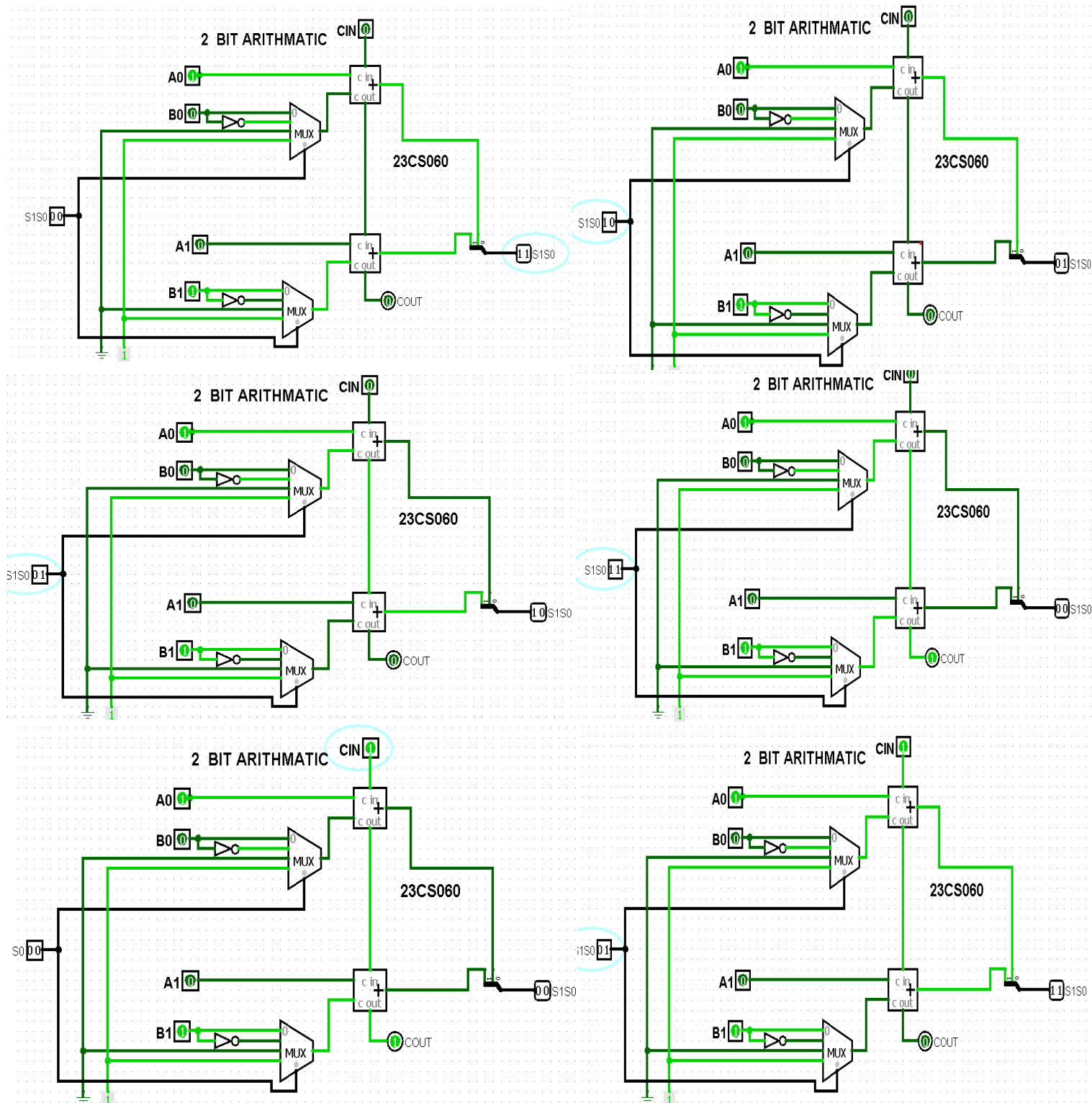







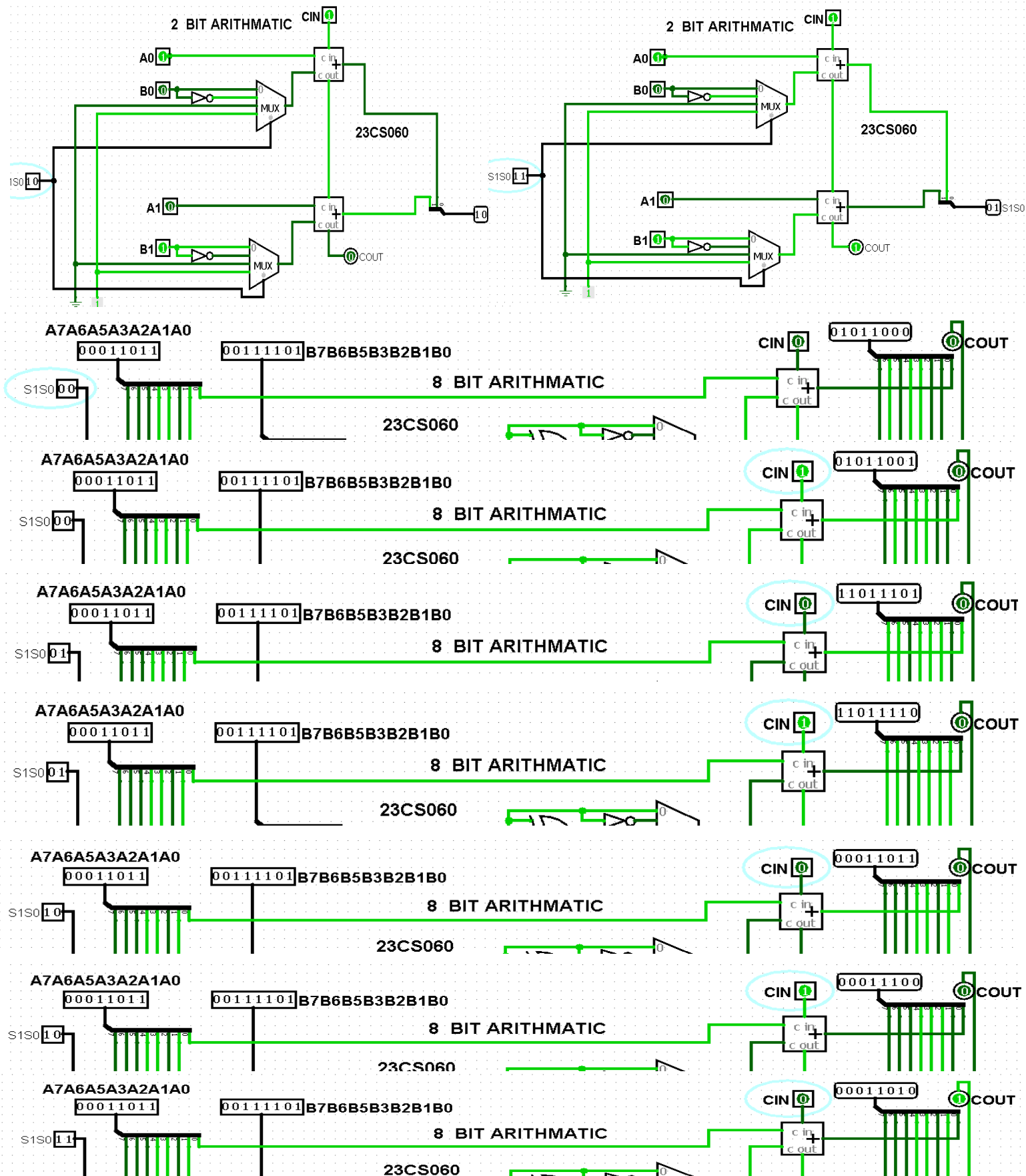


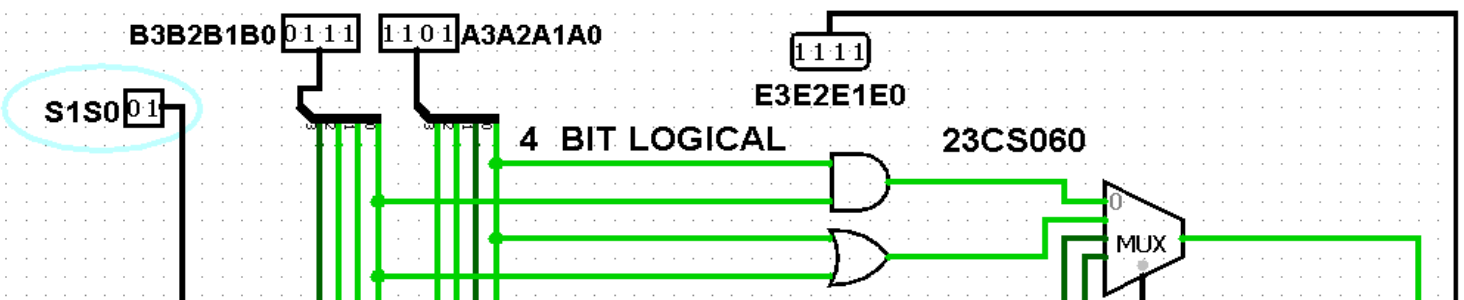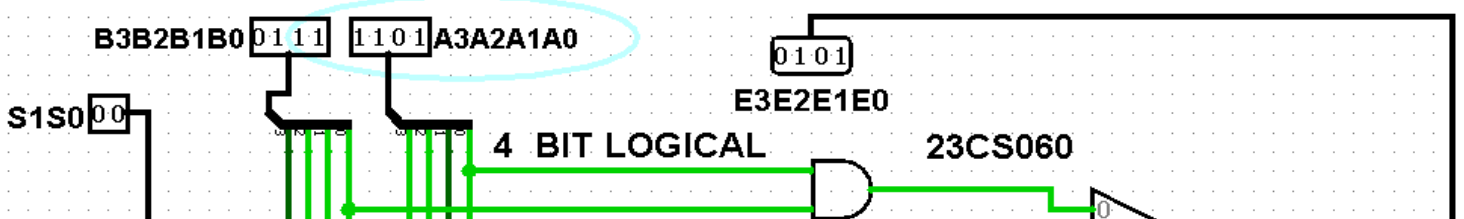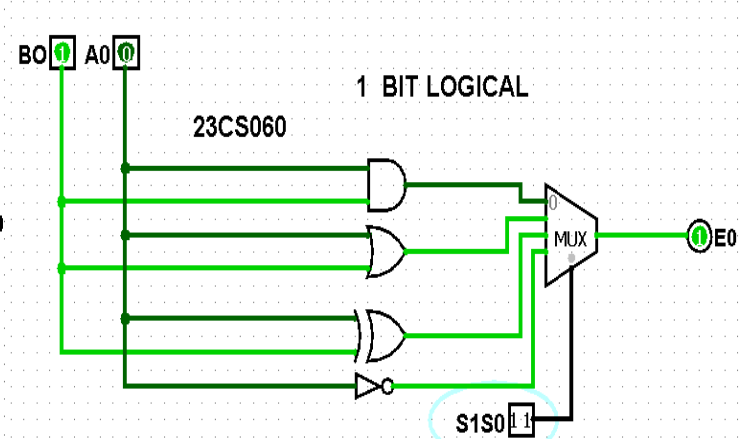
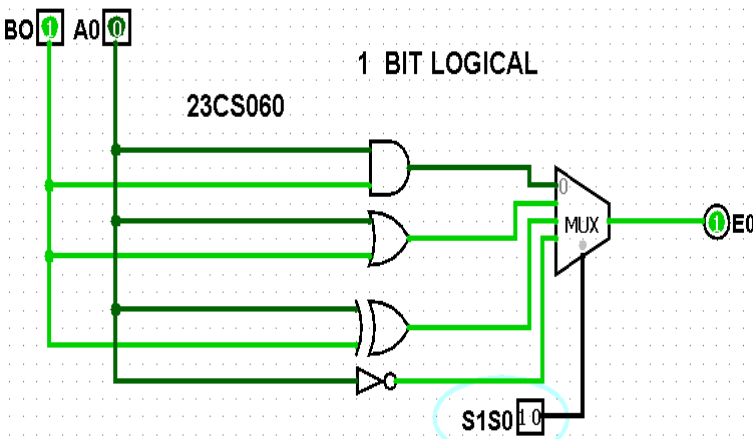
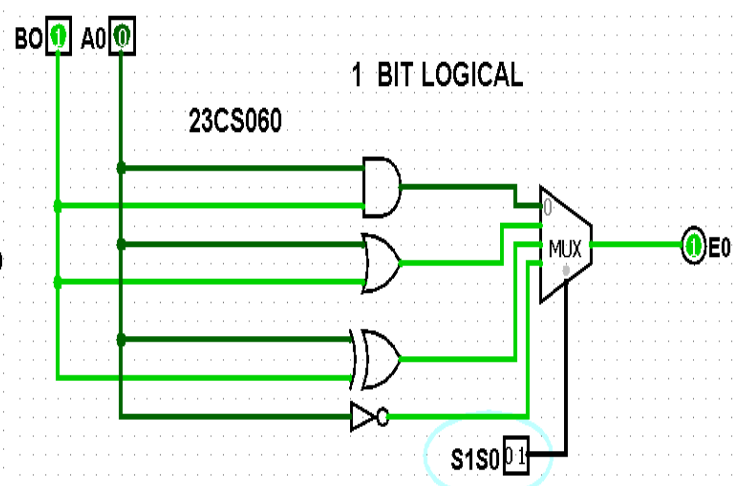
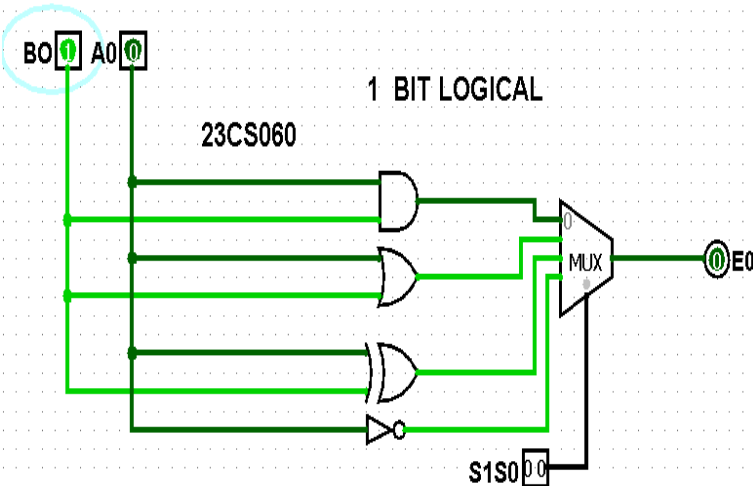



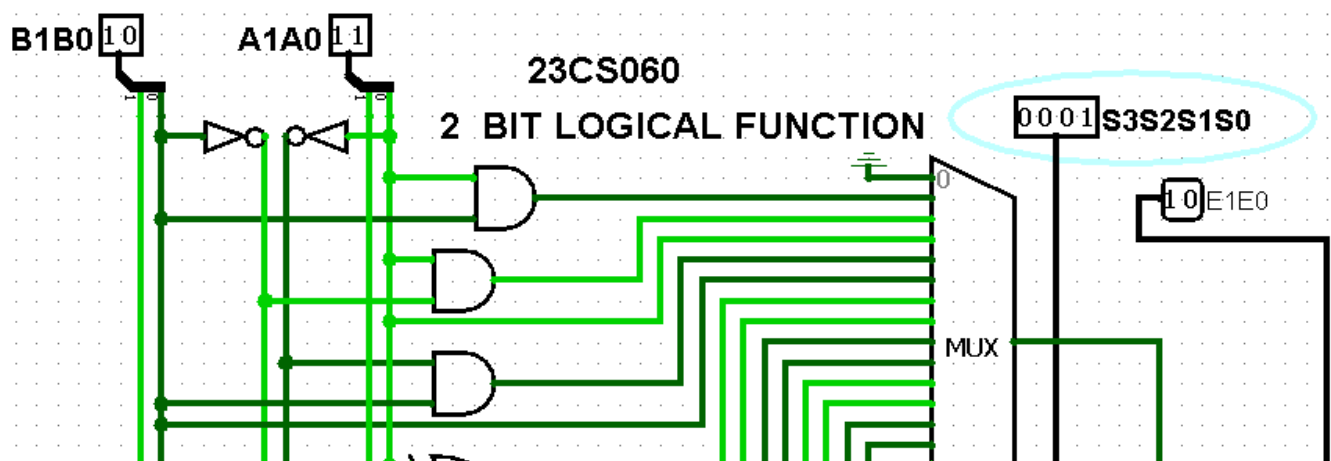
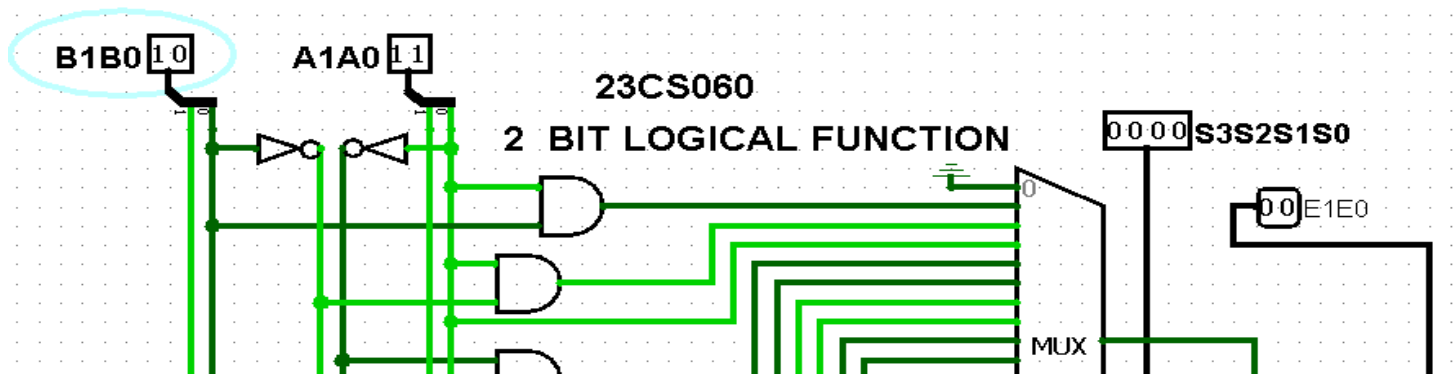
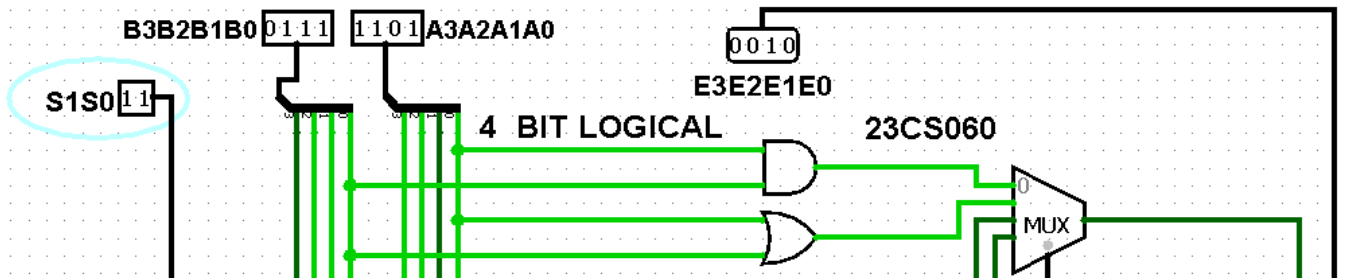
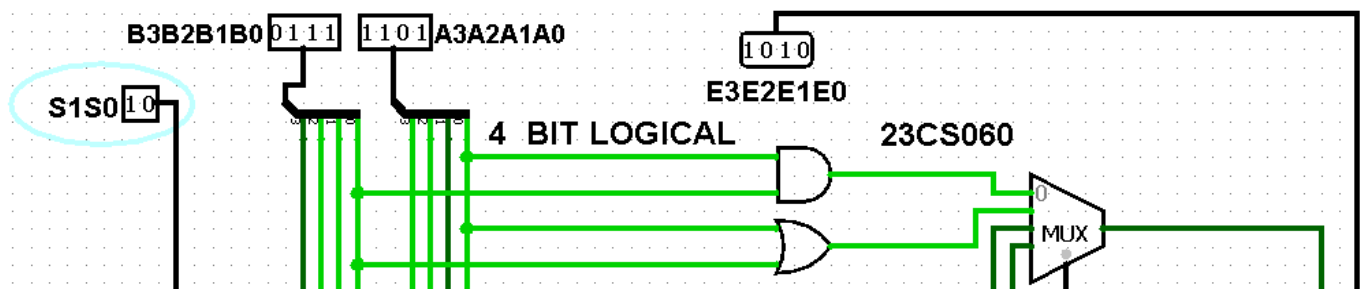


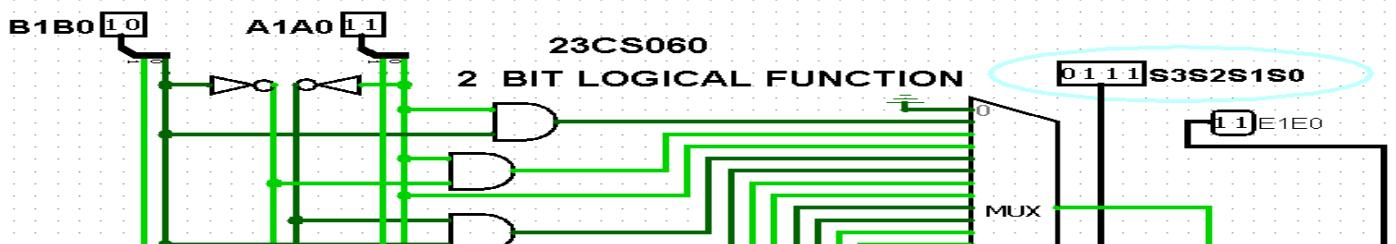
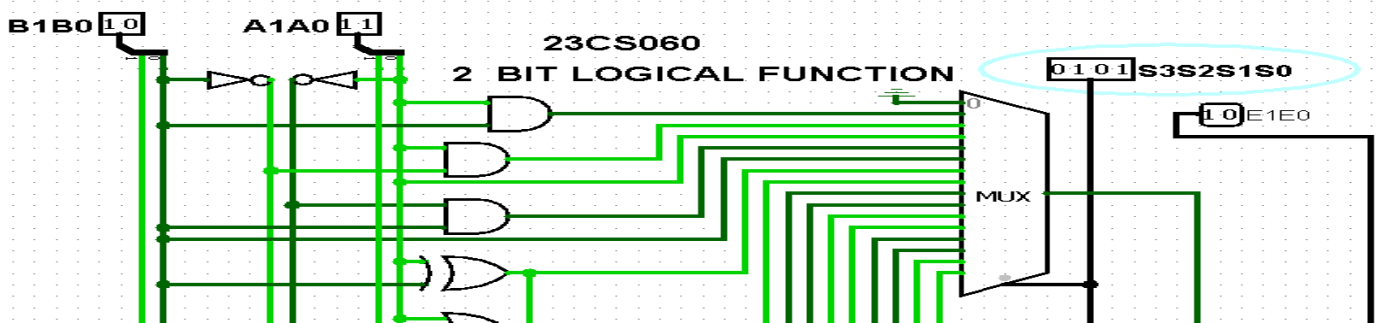
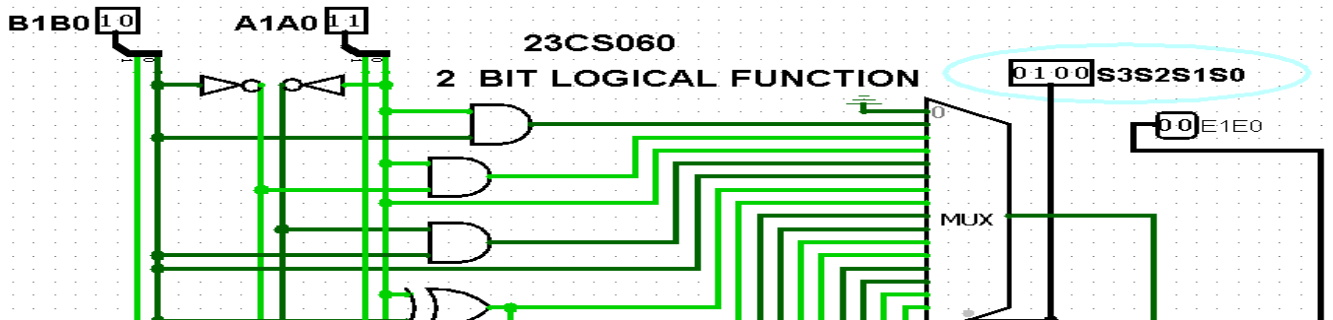
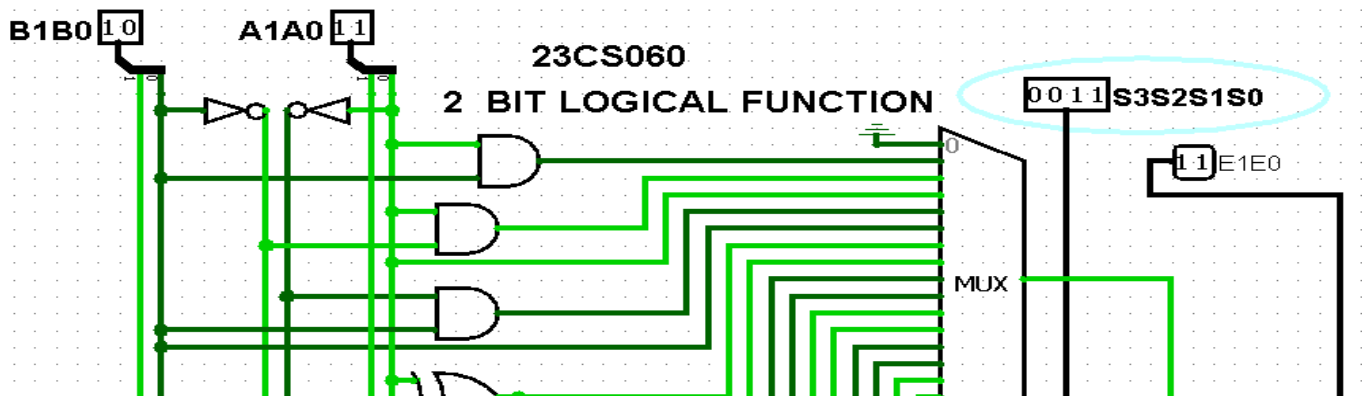
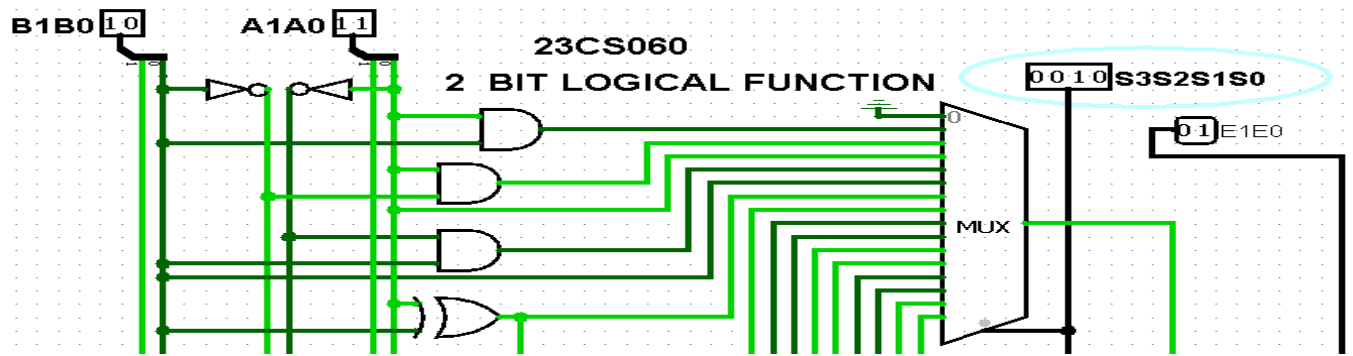







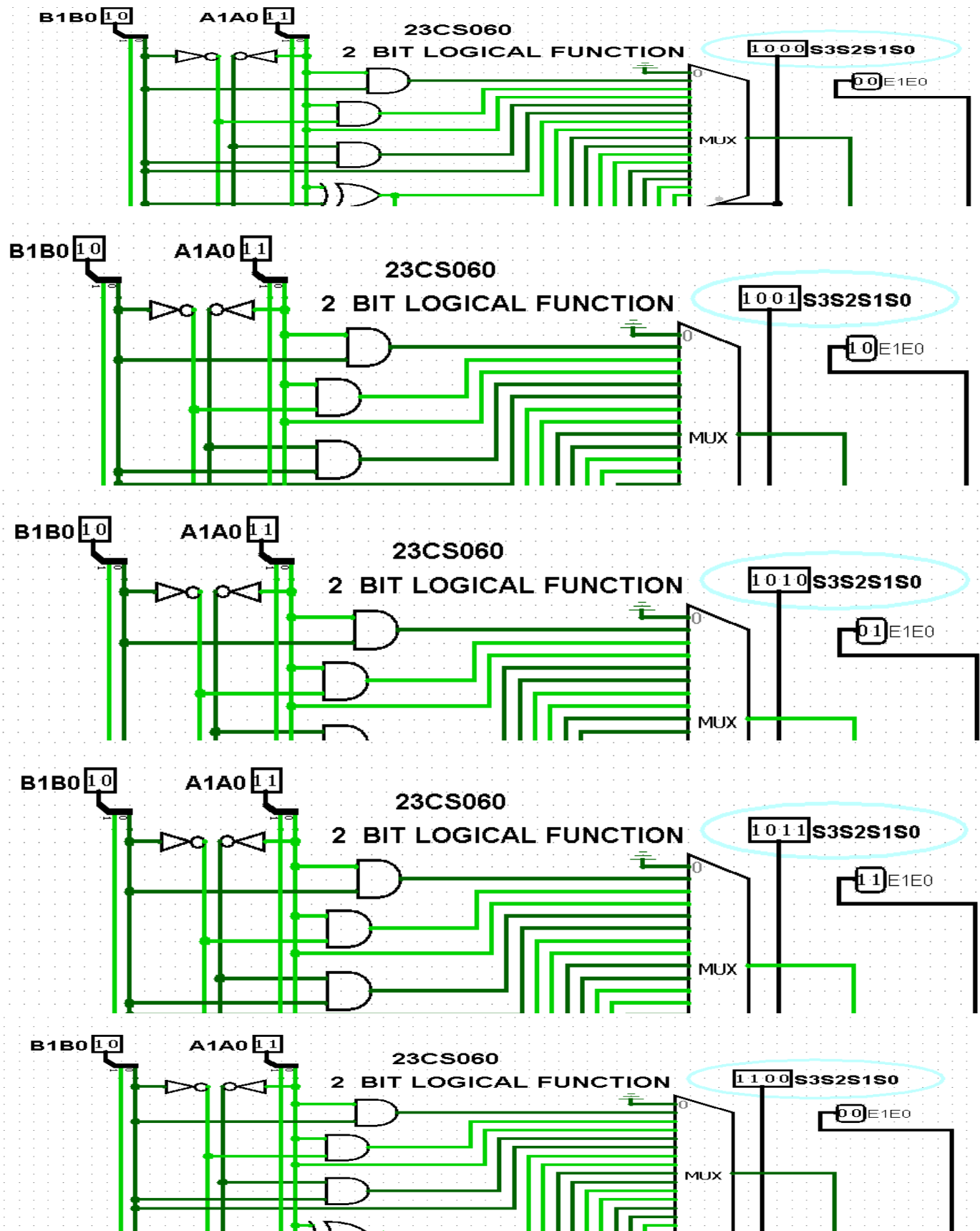


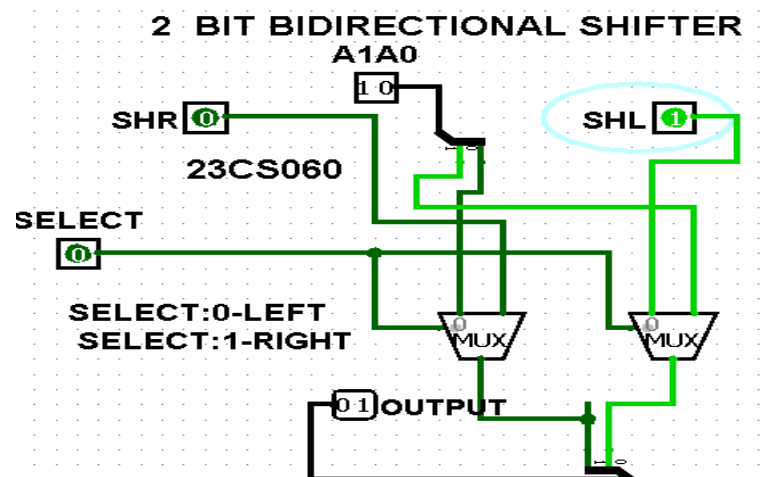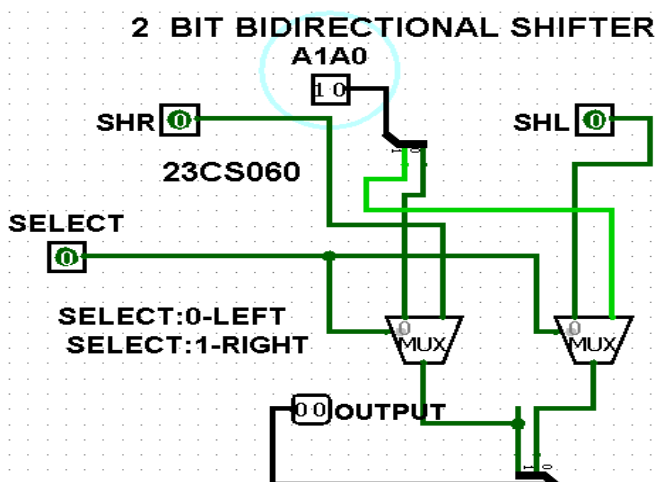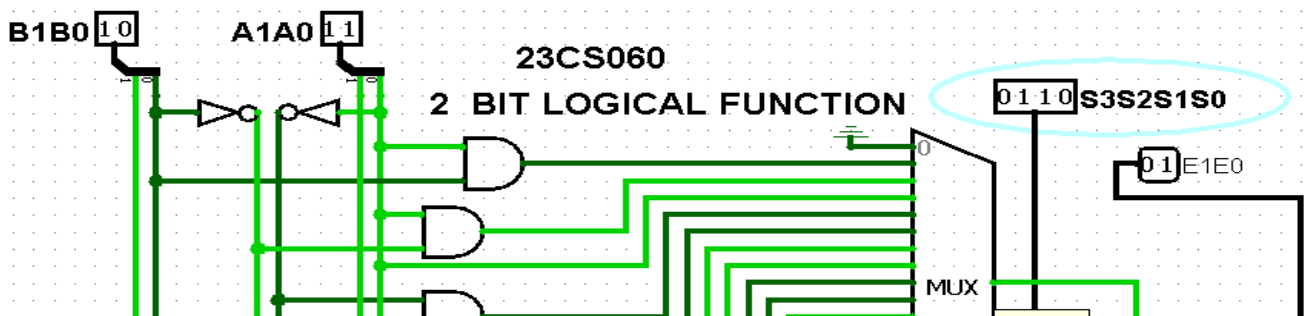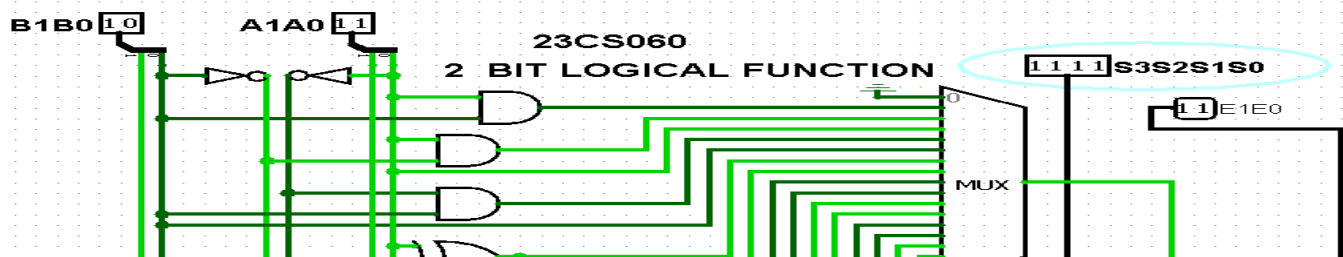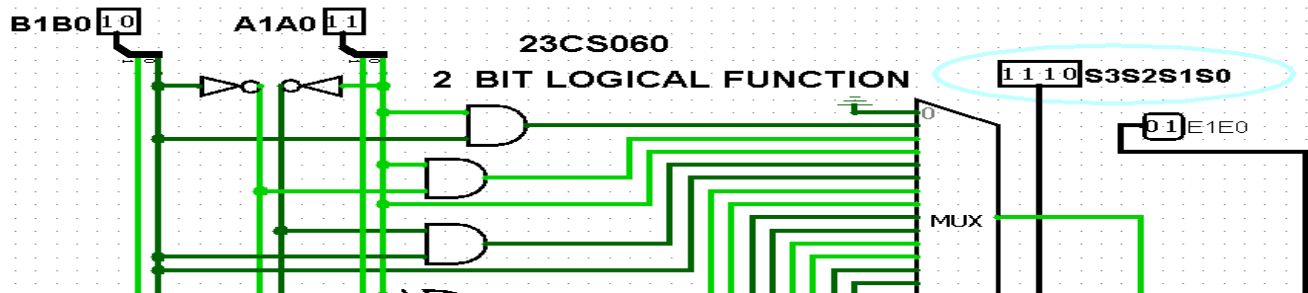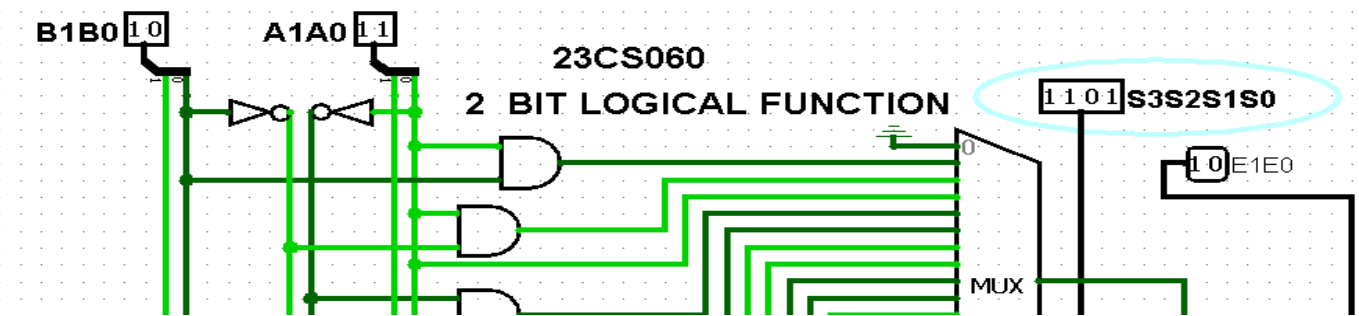


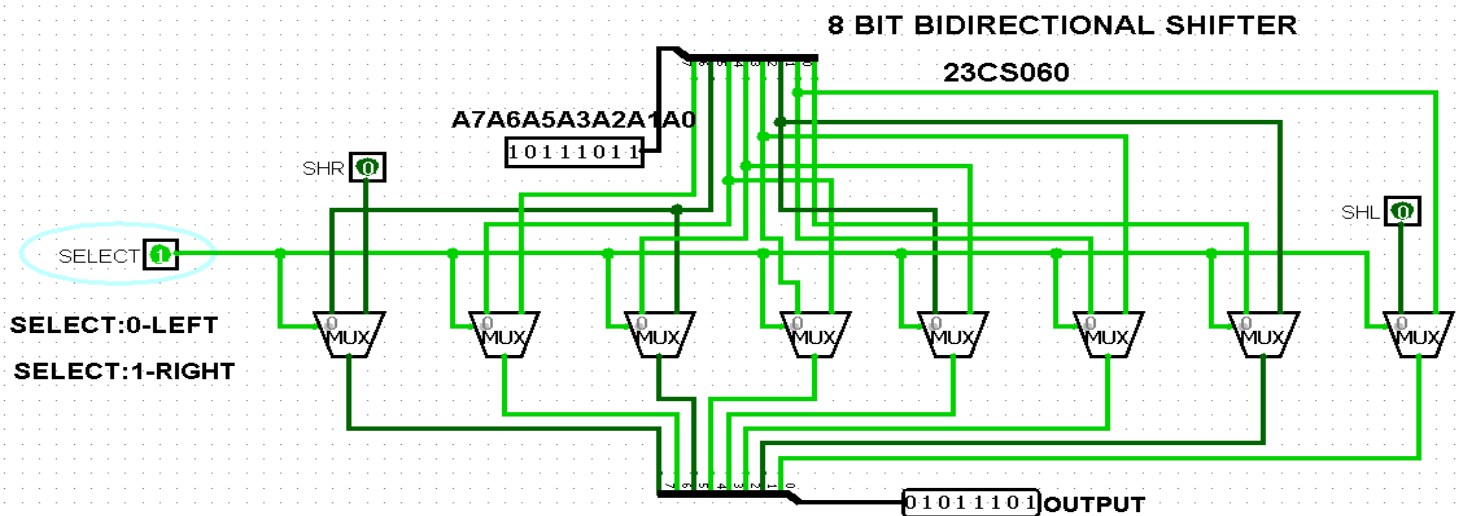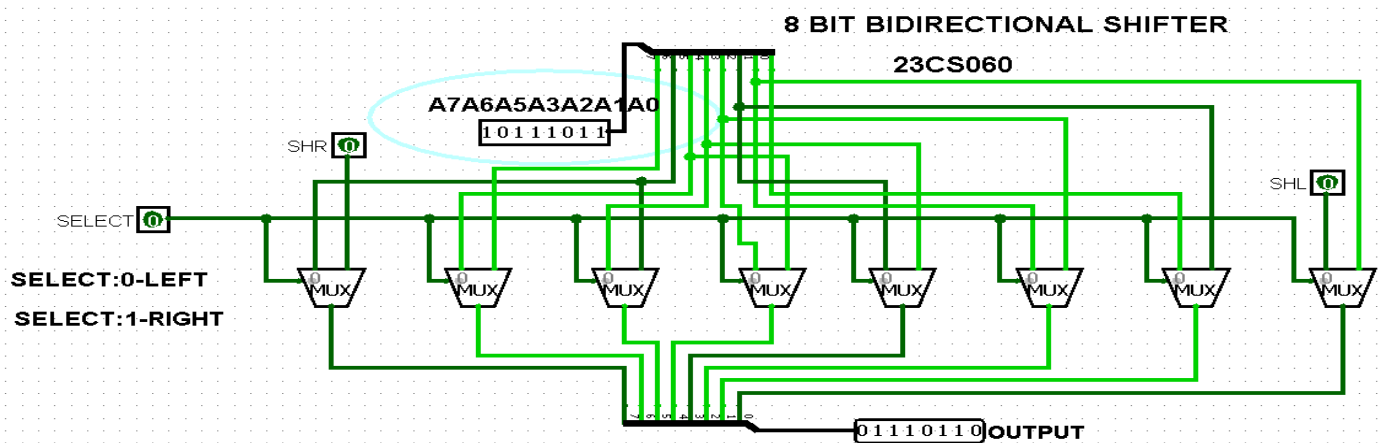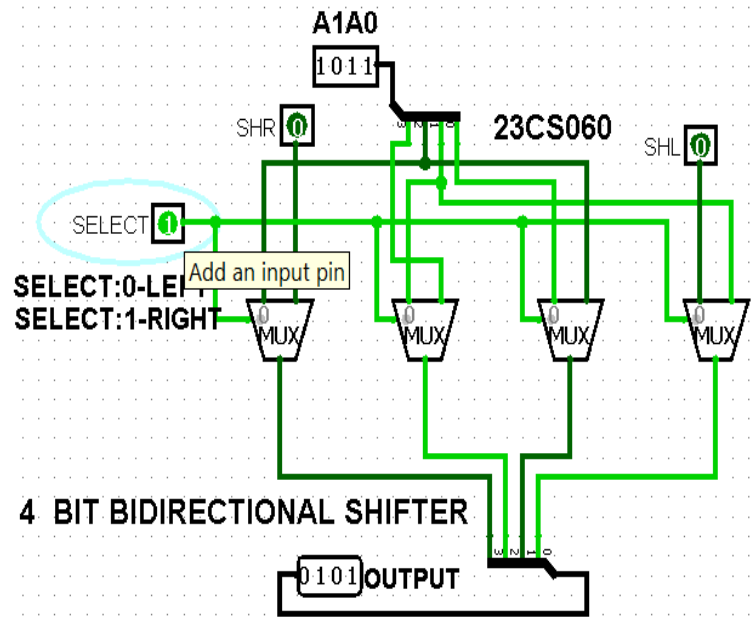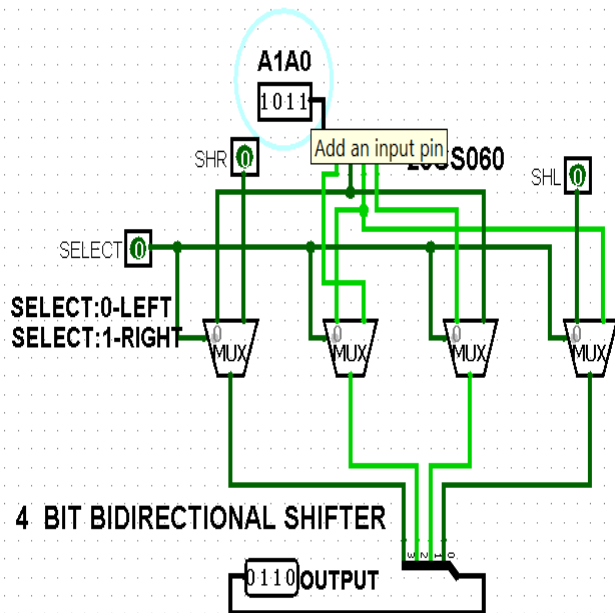


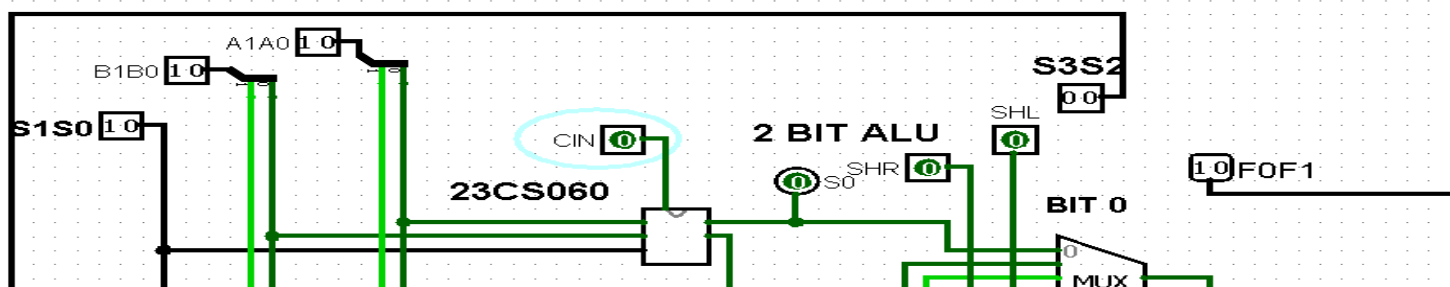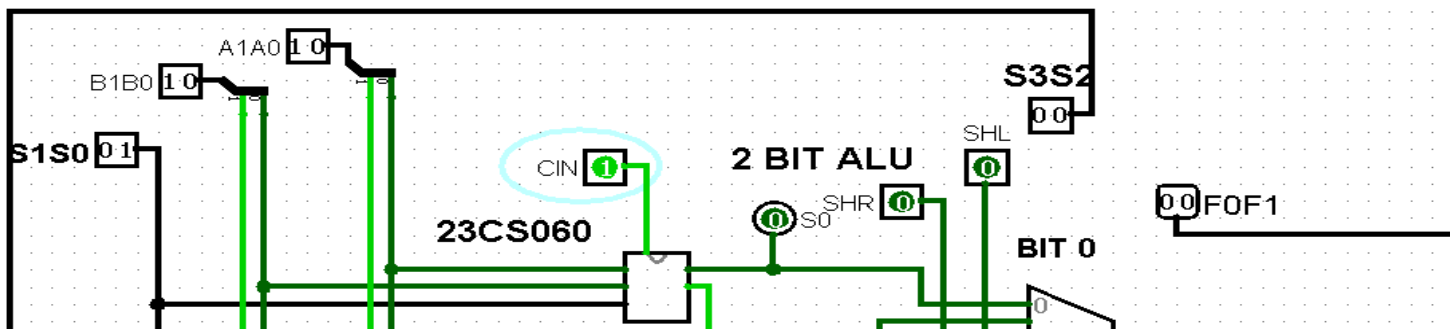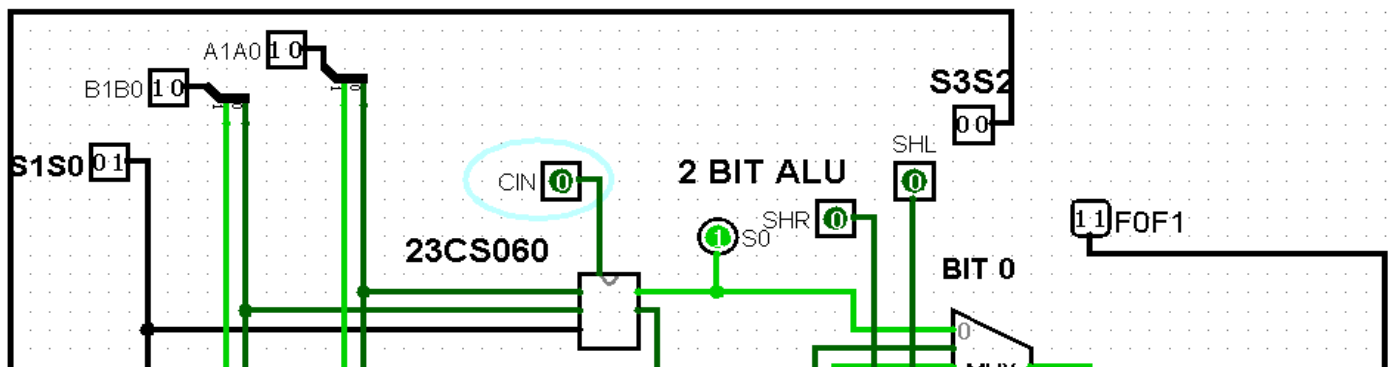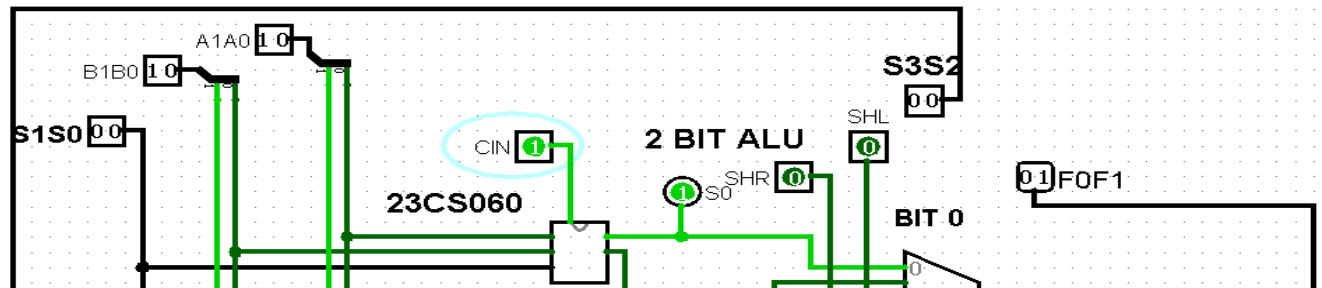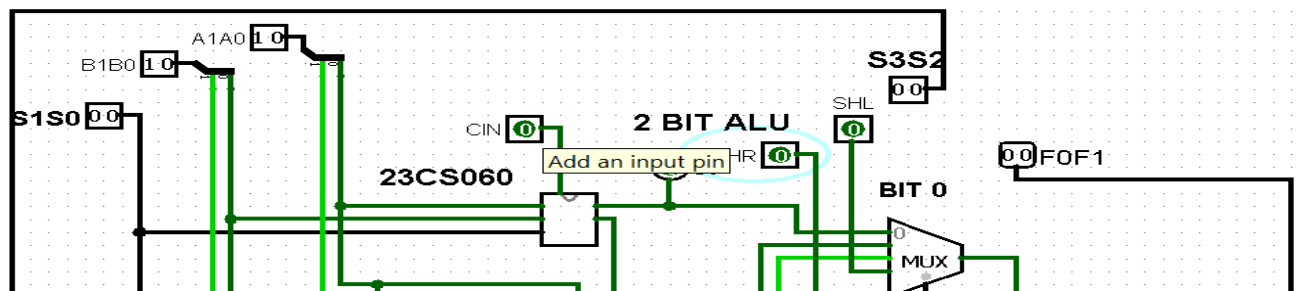

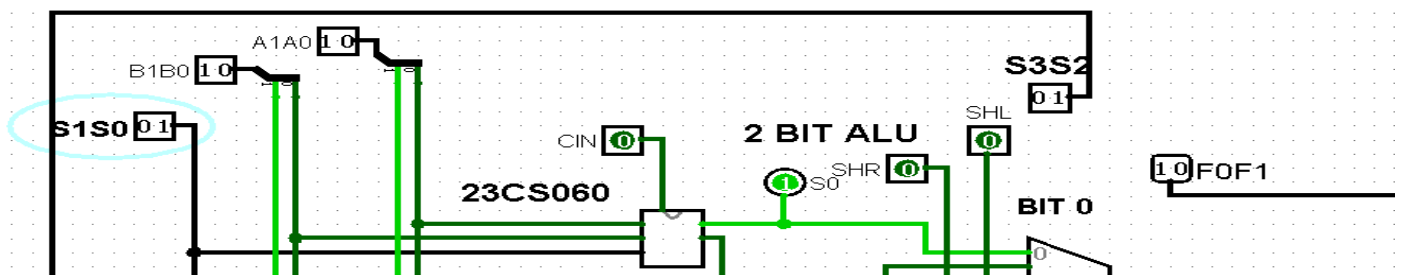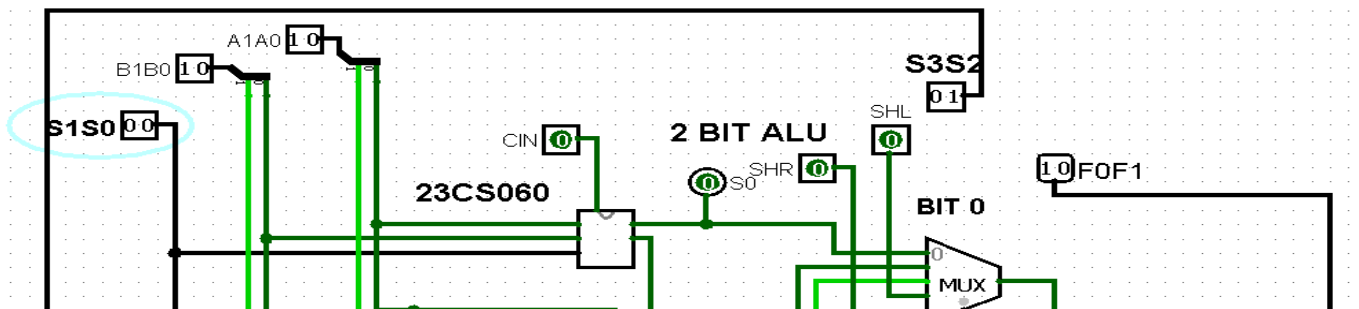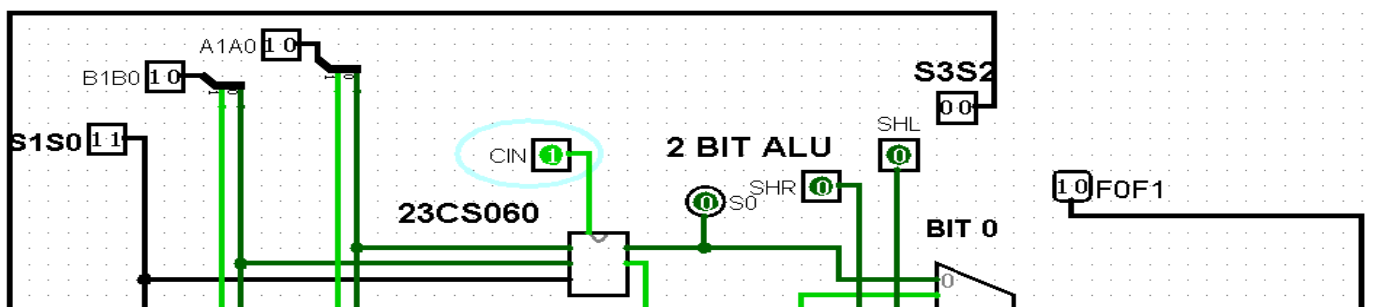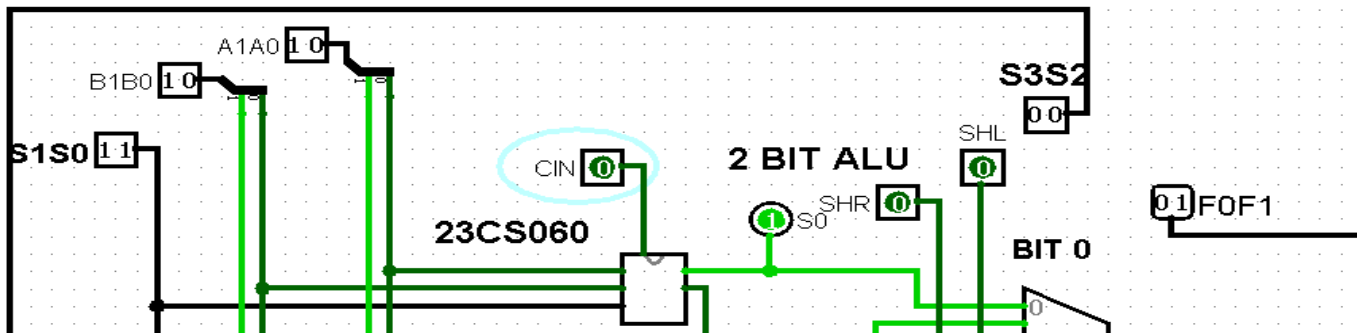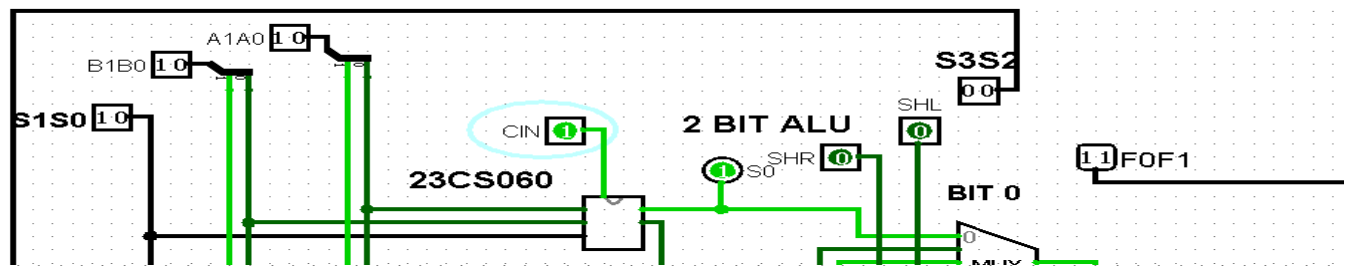

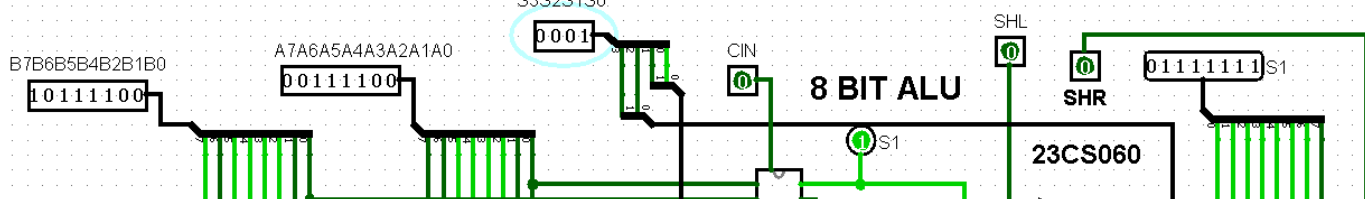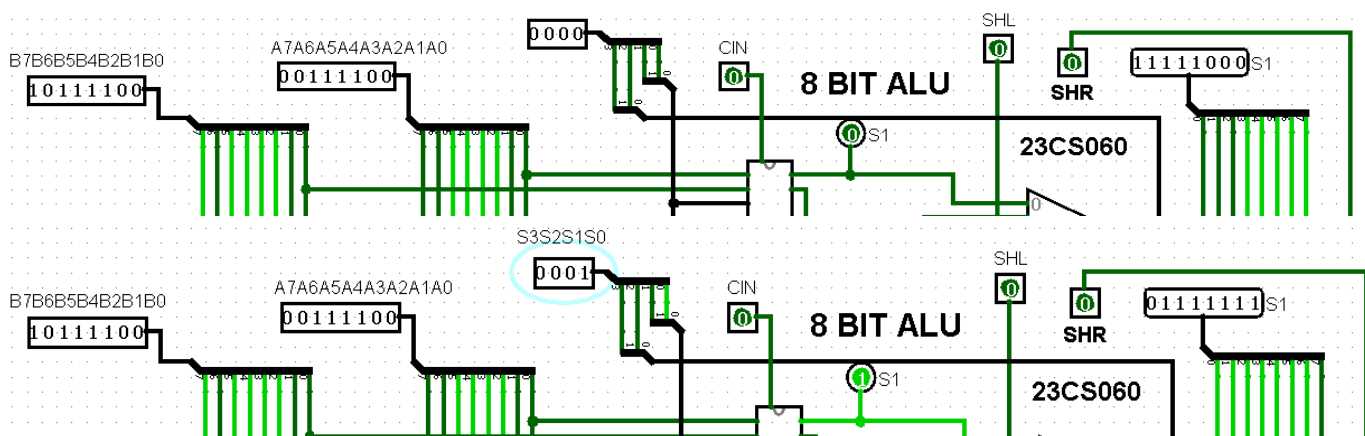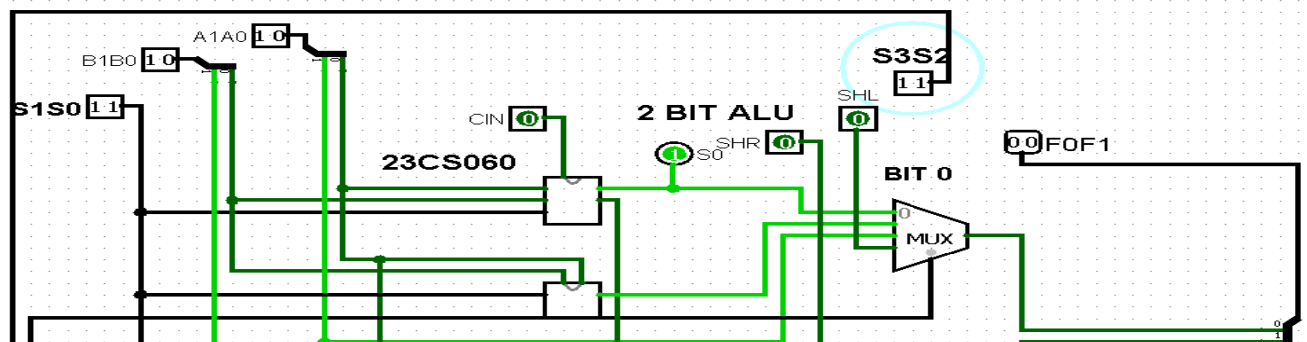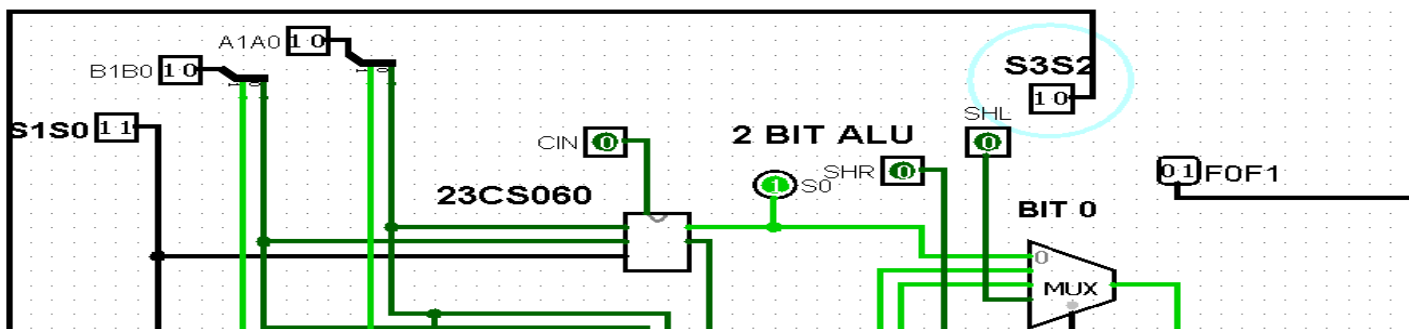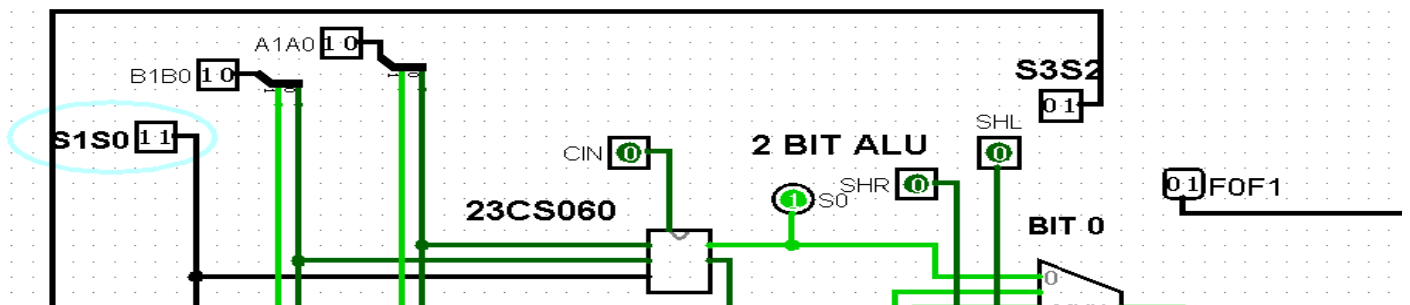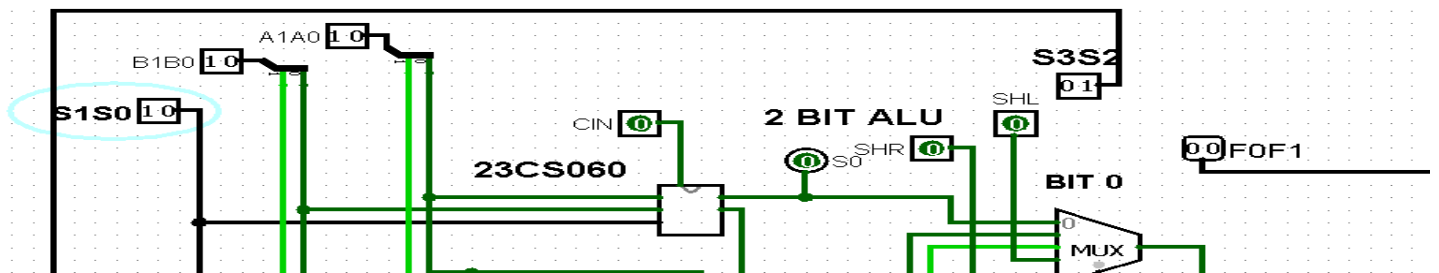

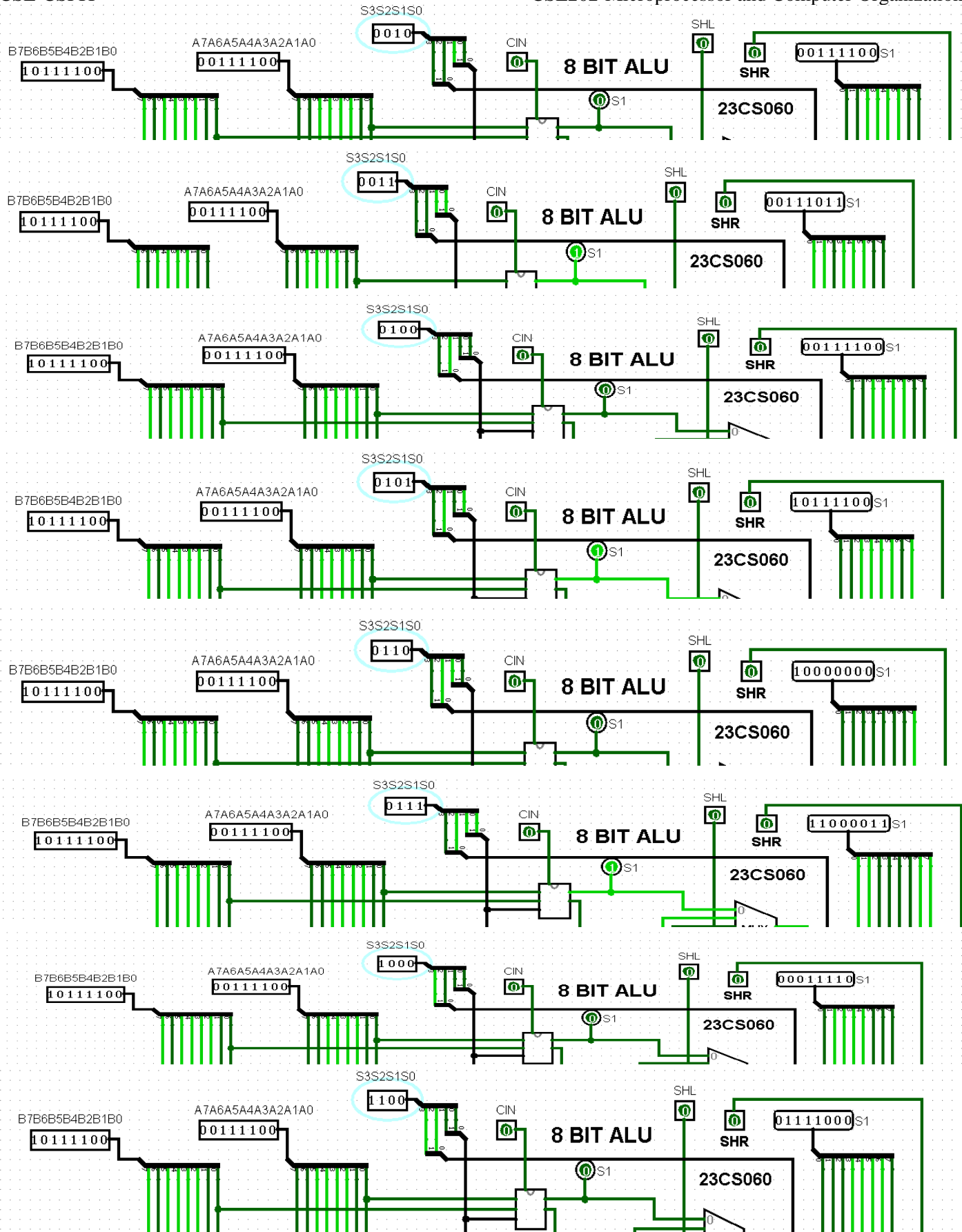

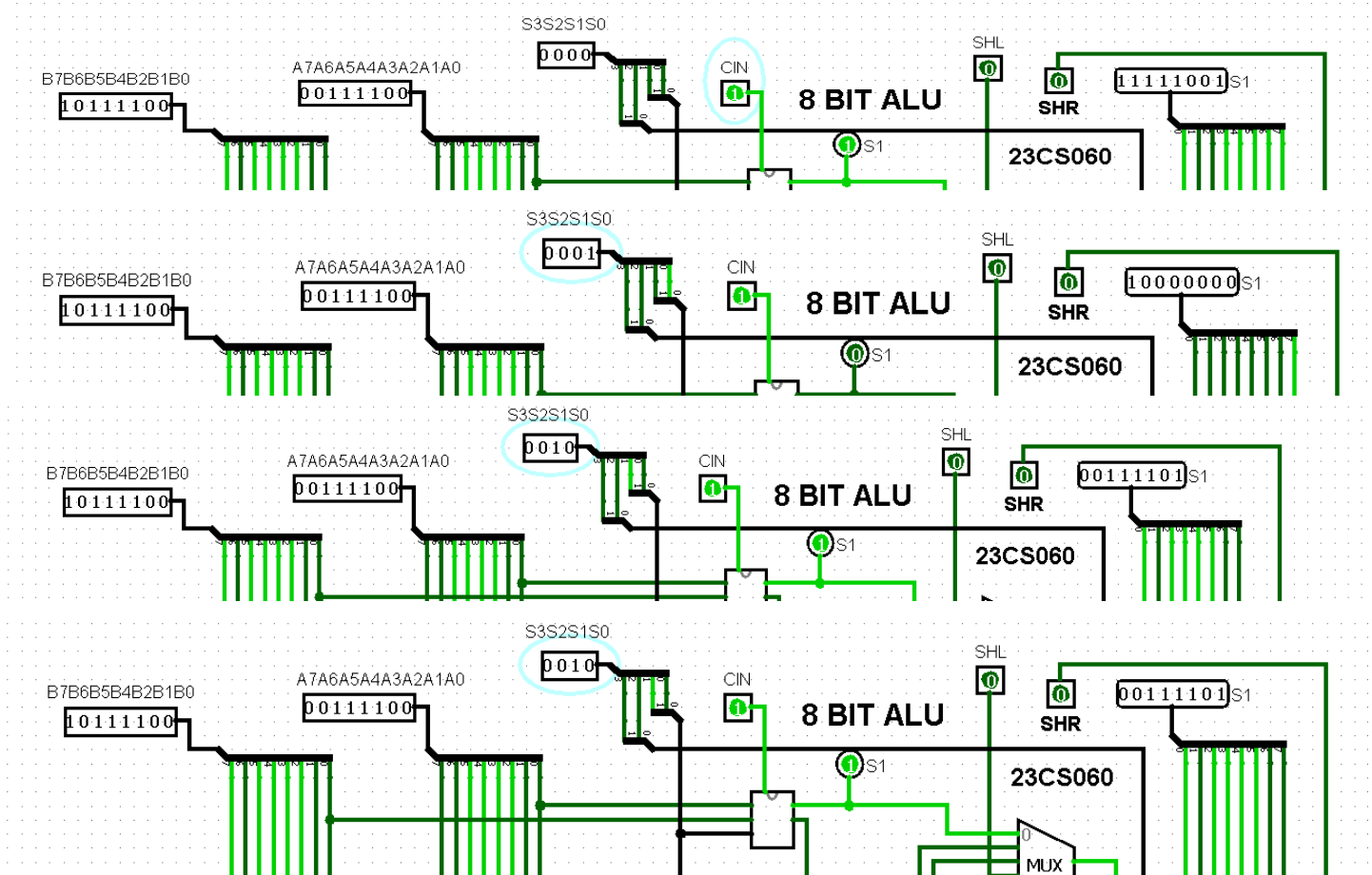

Conclusion: