


Date:

## **EXPERIMENT NO. 2**


**AIM: Implement a circuit in Logisim which perform Addition and Subtraction of sign number.**



**ALGORITHM:**



## CIRCUITS:


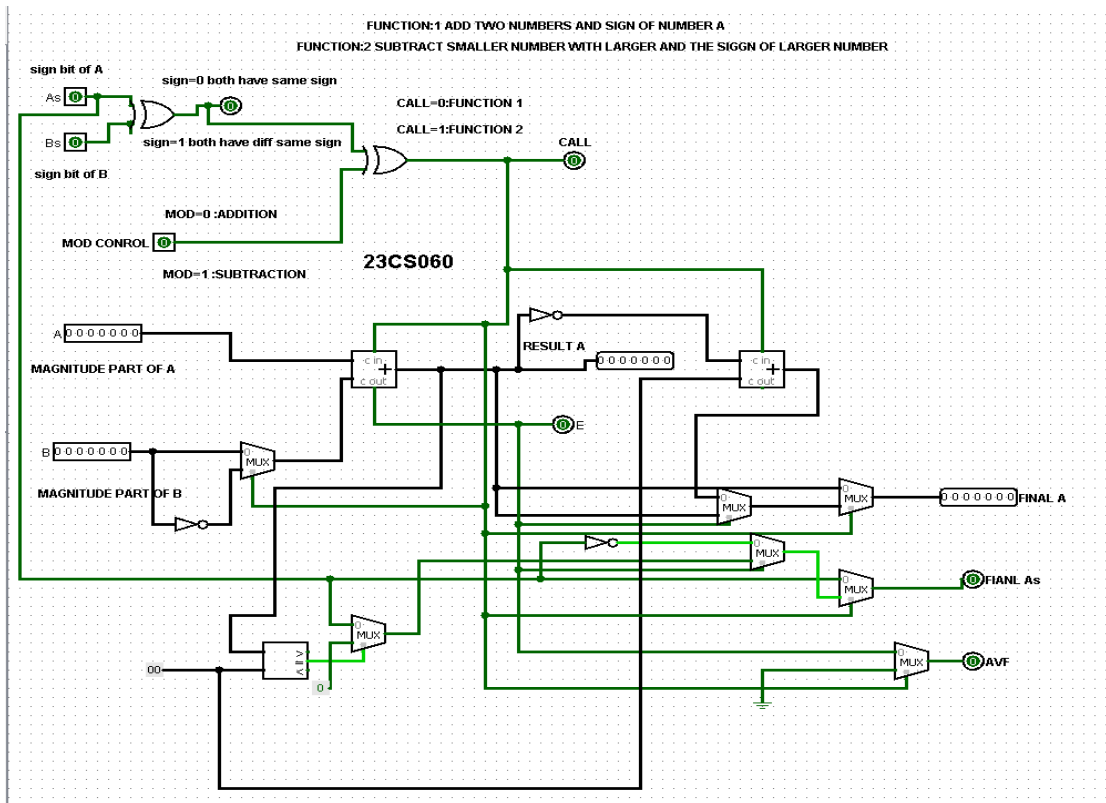



## OUTPUTS

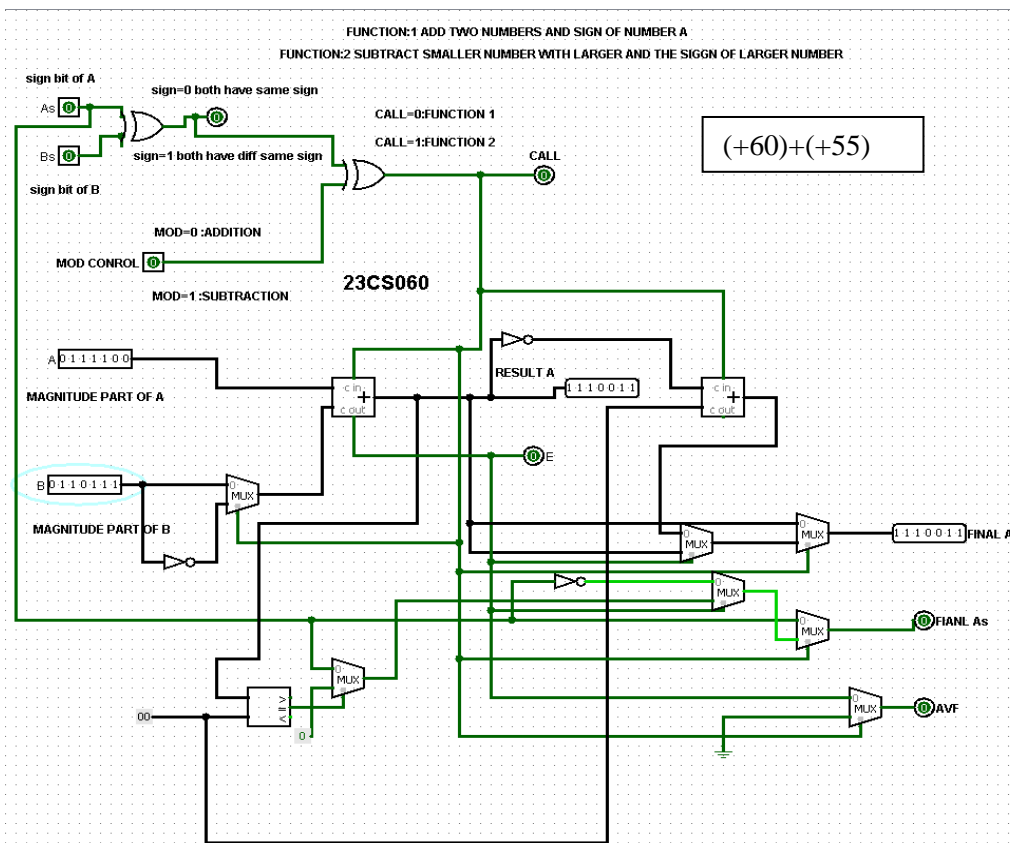

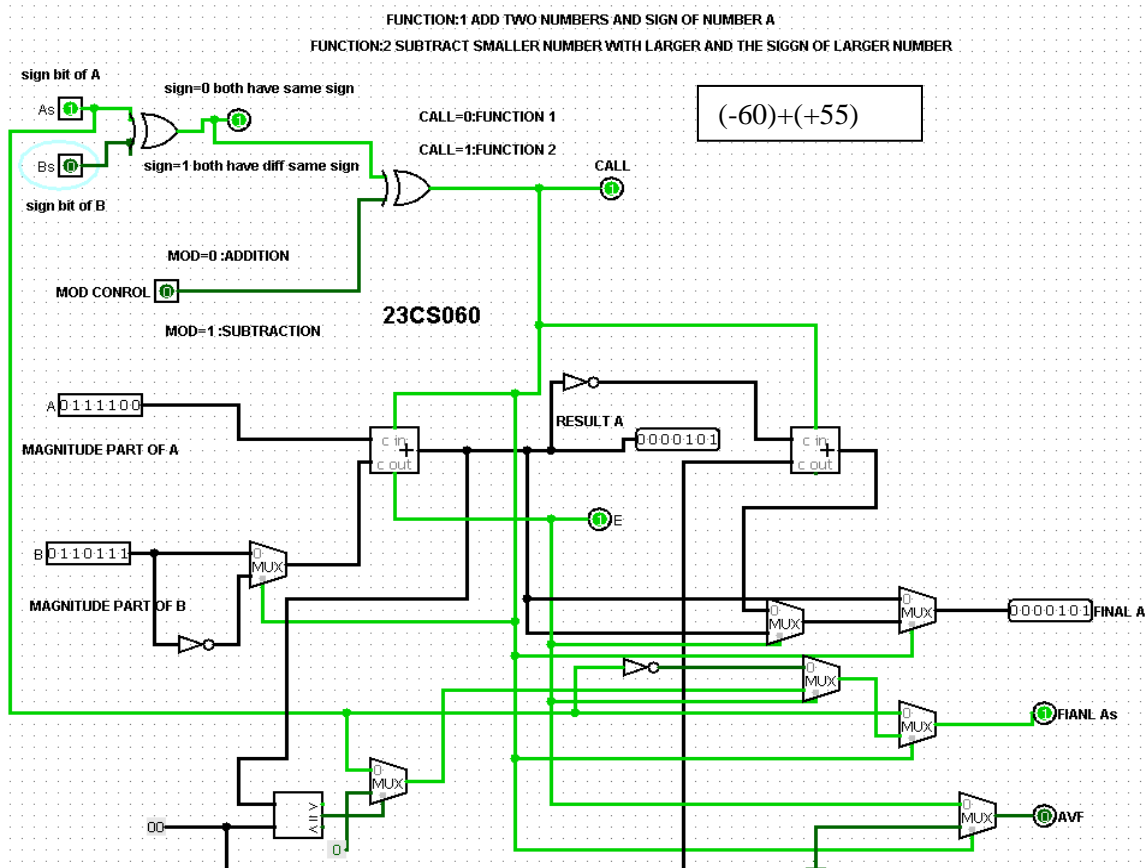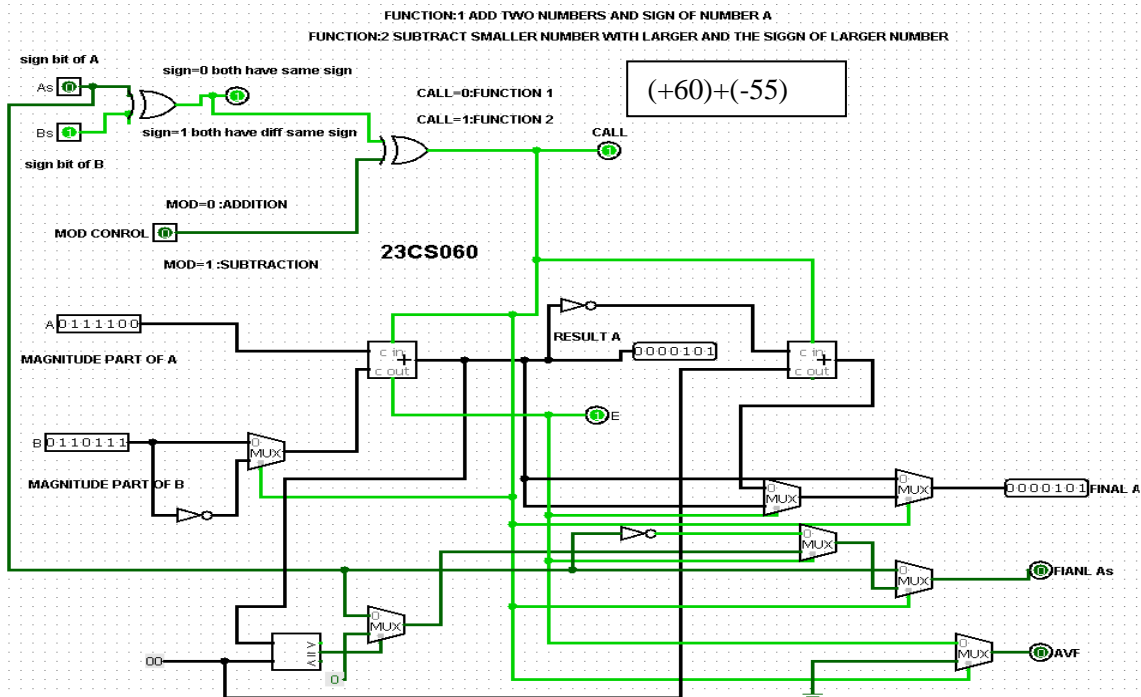

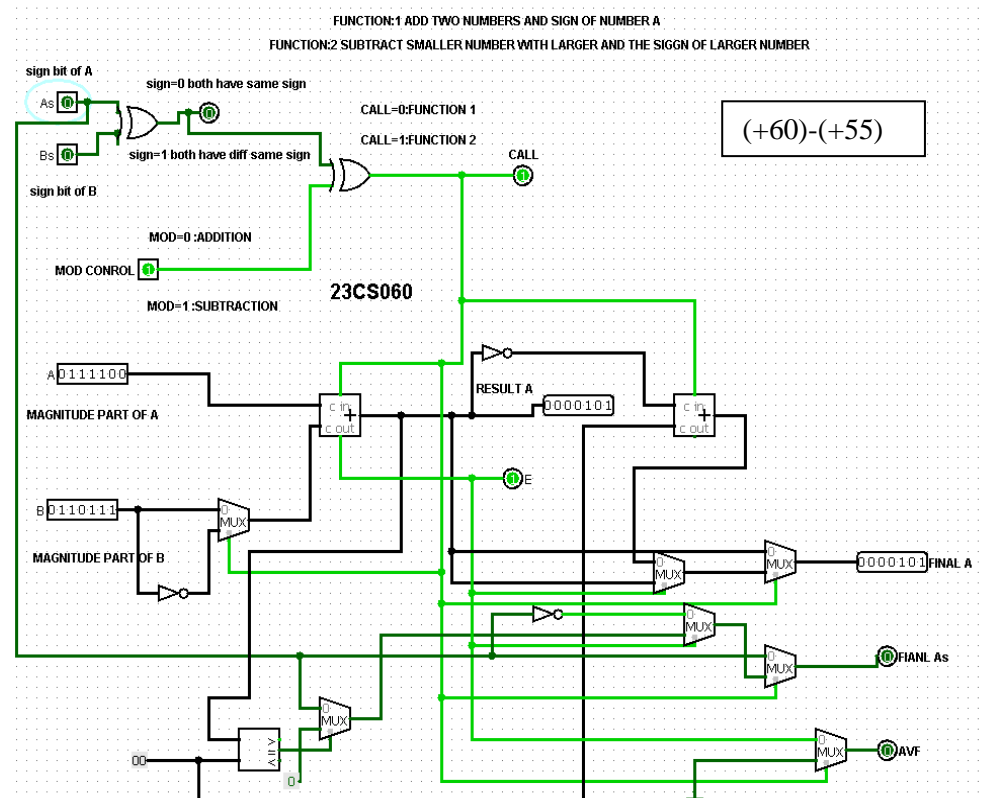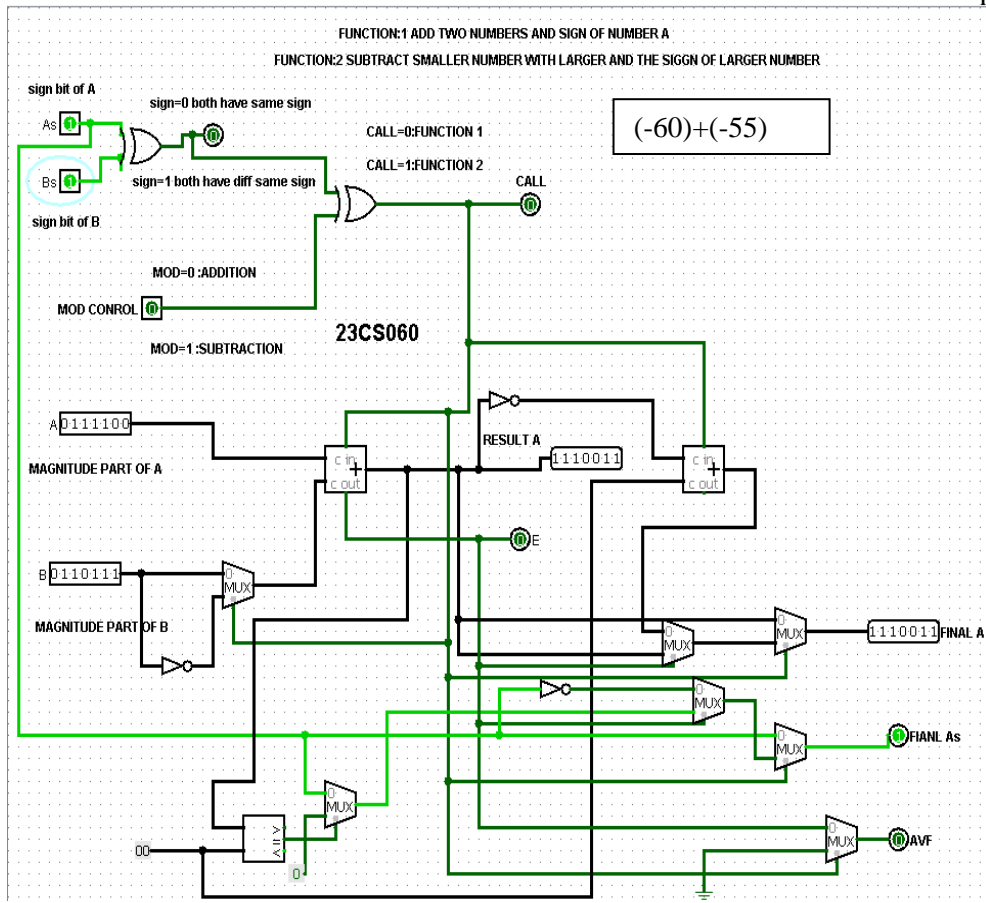

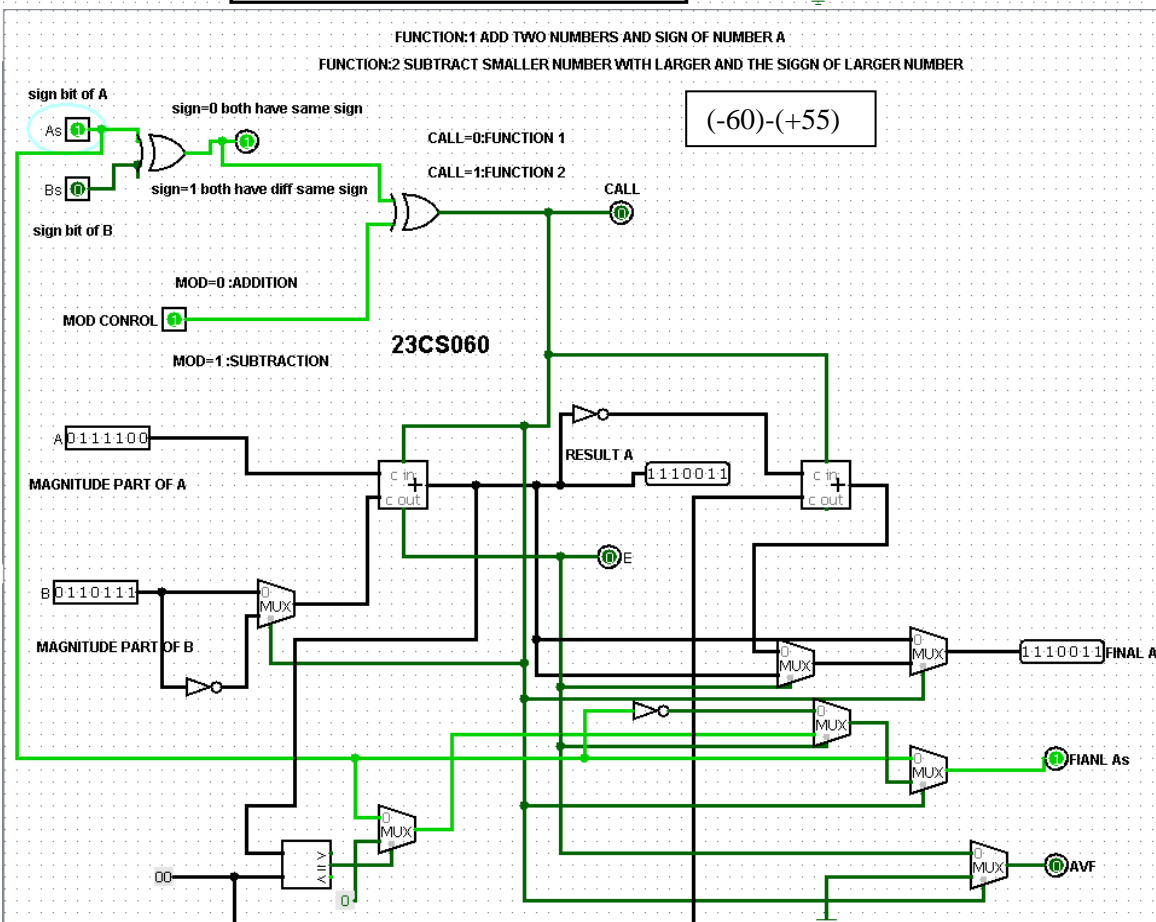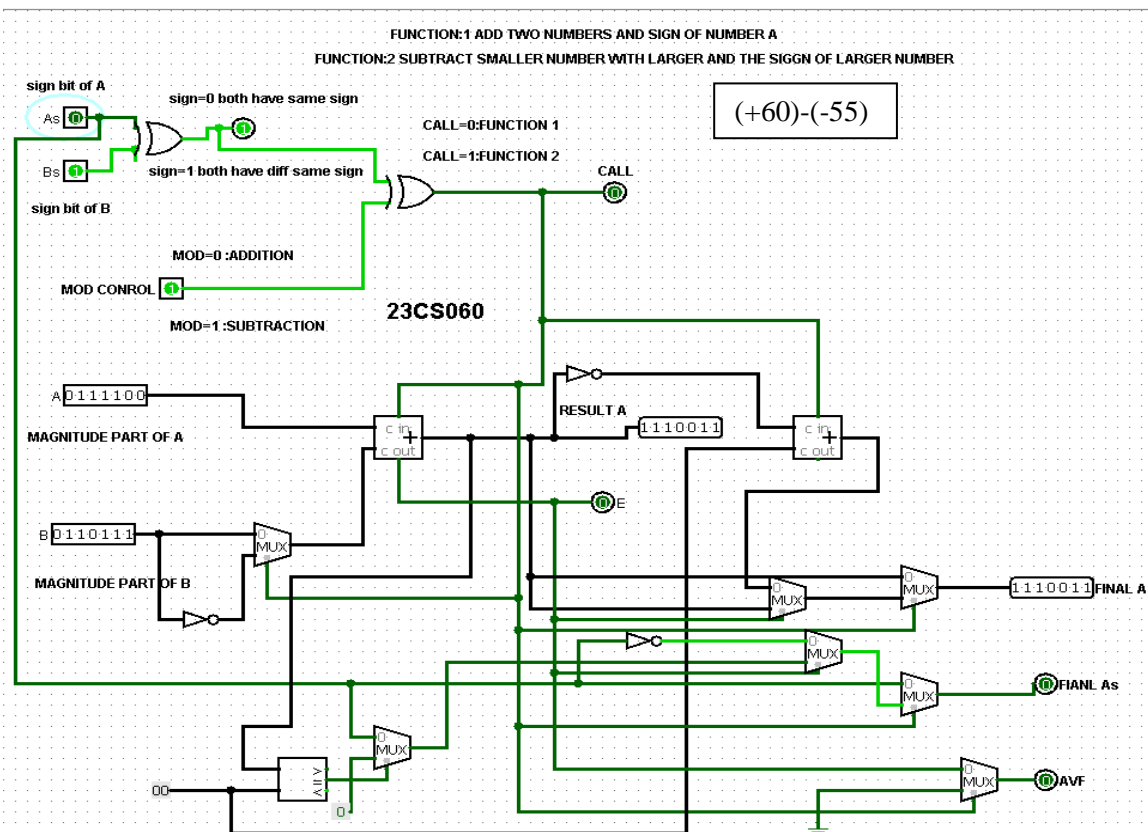

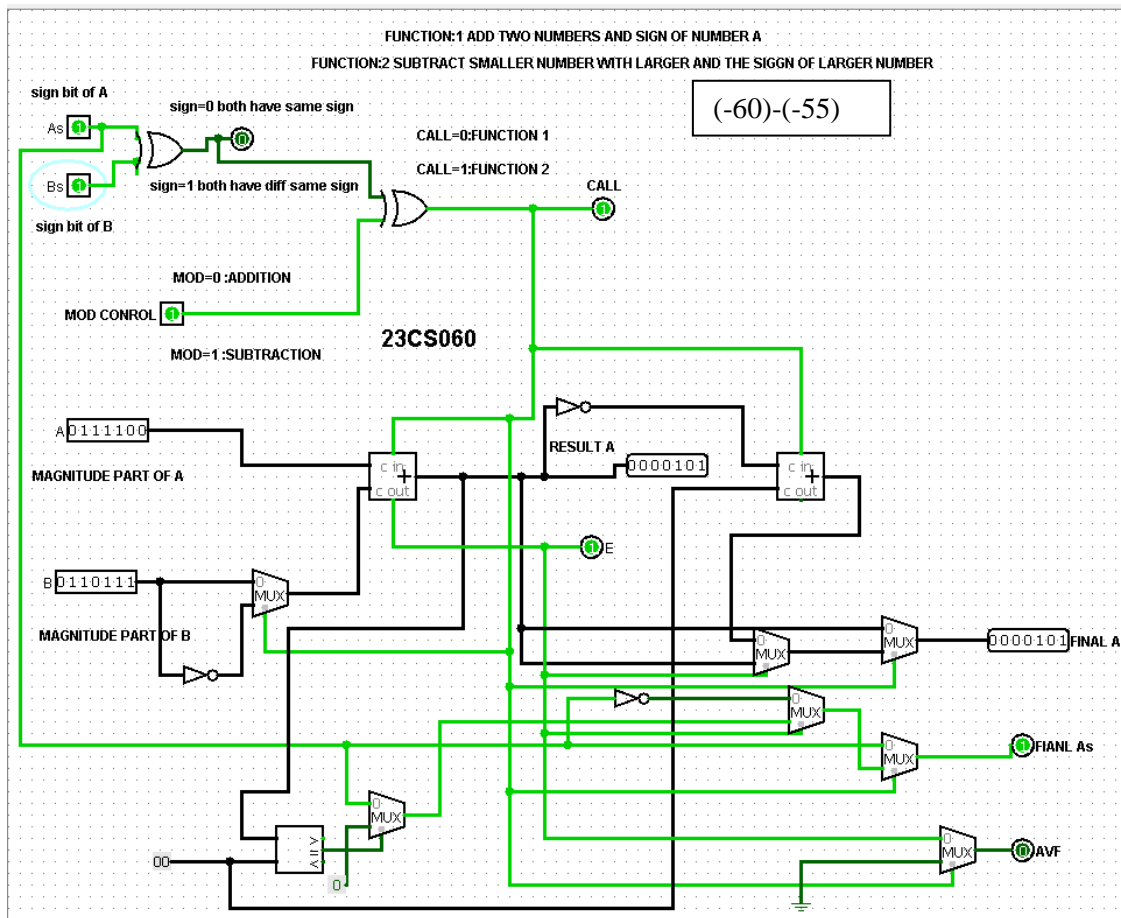

CONCLUSION: